

# **EE / CE – 211**

# **Basic Electronics**

## **(Spring – 2024)**

**Ahmad Usman**

| Ph.D. | Senior Member, IEEE |

Electrical & Computer Engineering (ECE) Program

Dhanani School of Science and Engineering (DSSE)

Habib University



**DHANANI  
SCHOOL OF SCIENCE  
AND ENGINEERING**

- **Reading for this Lecture**

- Chapter # 4 and 5 of **“Introduction to Microelectronics”** by Behzad Razavi
- Chapter # 10 of **“Semiconductor Device Fundamentals”** by R.F. Pierret


# Physics of Bipolar Junction Transistors

## ☐ What we shall be doing in this chapter


- ☐ Voltage-Controlled Device as an Amplifier
- ☐ Structure of Bipolar Junction Transistor (BJT)
- ☐ Operation of BJT
- ☐ Large-Signal Model of BJT
- ☐ Small-Signal Model of BJT

# Physics of Bipolar Junction Transistors

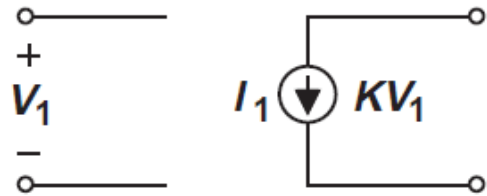
## □ Voltage-dependant Current Source and Amplifier



(a)

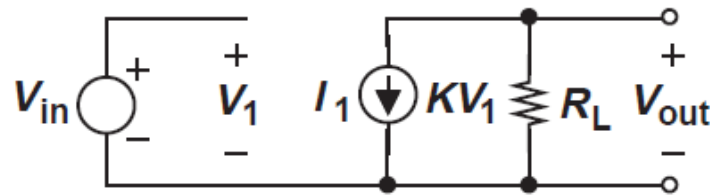

(b)

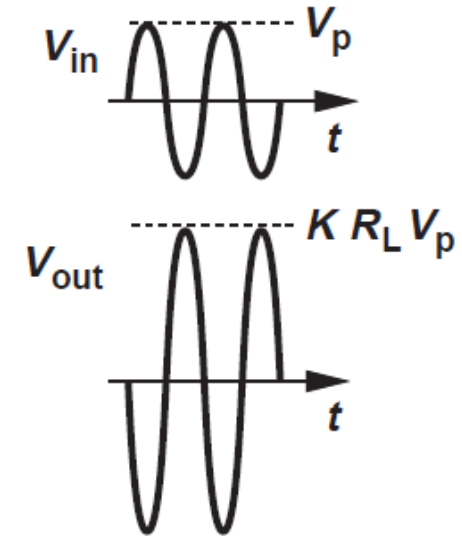

**Figure 4.1** (a) Voltage-dependent current source, (b) simple amplifier.

# Physics of Bipolar Junction Transistors

## Example 4.1

Consider the circuit shown in Fig. 4.2, where the voltage-controlled current source exhibits an “internal” resistance of  $r_{in}$ . Determine the voltage gain of the circuit.


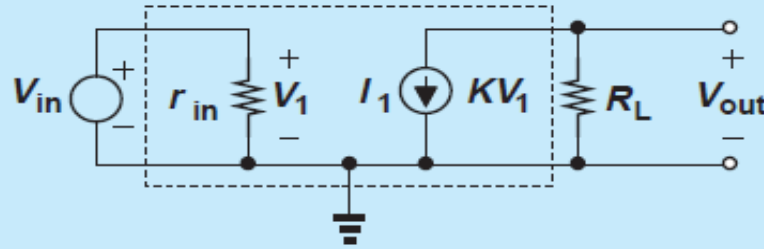



Figure 4.2 Voltage-dependent current source with an internal resistance  $r_{in}$ .

# Physics of Bipolar Junction Transistors

## □ Structure of Bipolar Junction Transistors (BJTs)

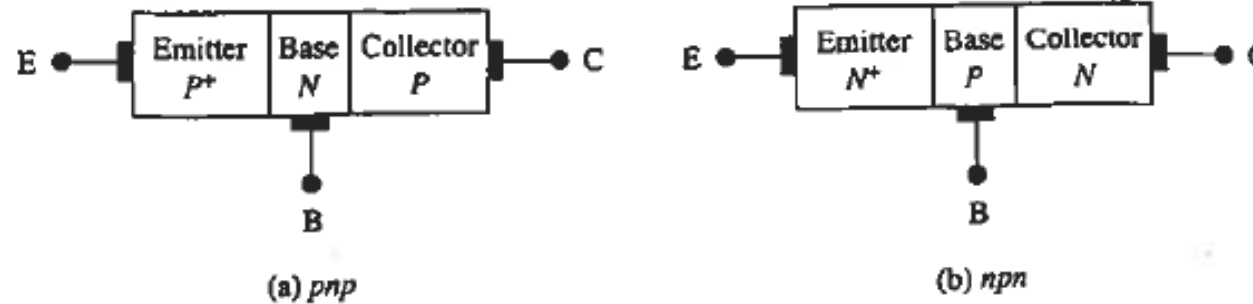

**Figure 10.1** Schematic representation of the (a) *pnp* and (b) *npn* BJT showing device regions and the terminal designations.

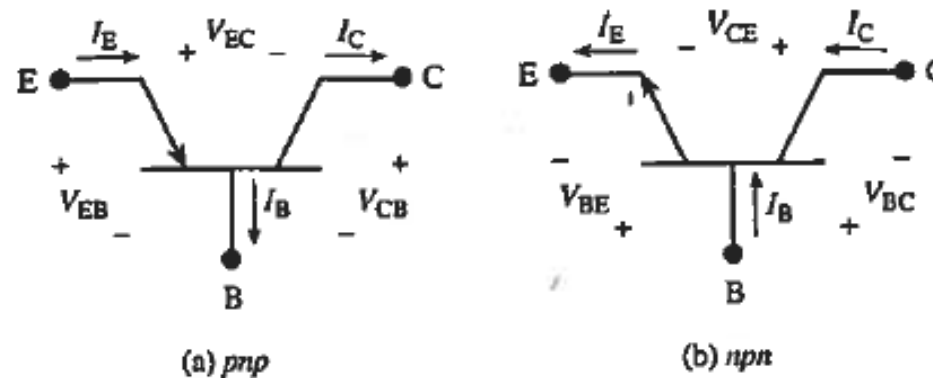

**Figure 10.2** (a) *pnp* and (b) *npn* BJT circuit symbols. The d.c. terminal currents, voltages, and reference polarities are also noted in the figure.

# Physics of Bipolar Junction Transistors

## □ Structure of Bipolar Junction Transistors (BJTs)


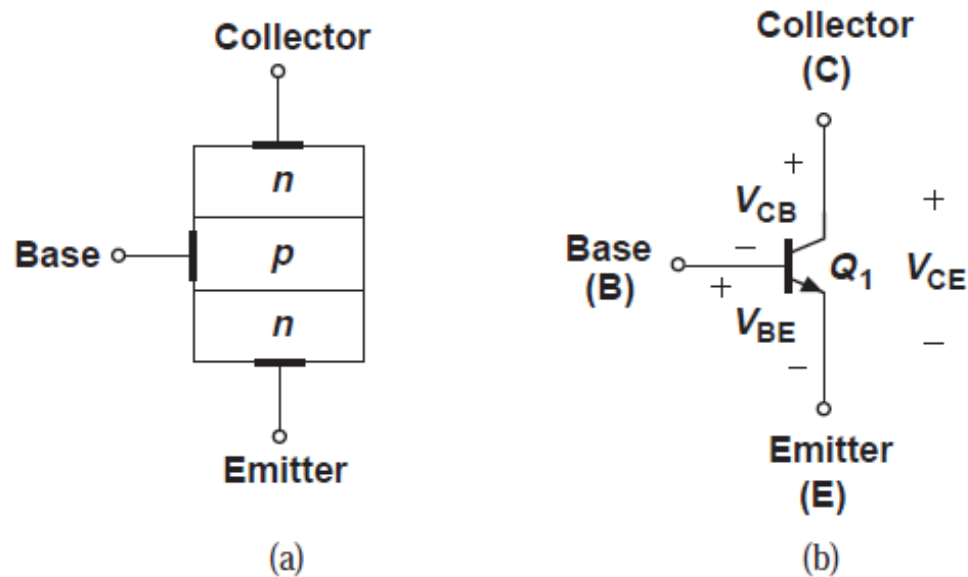


Figure 4.4 (a) Structure and (b) circuit symbol of bipolar transistor.

# Physics of Bipolar Junction Transistors
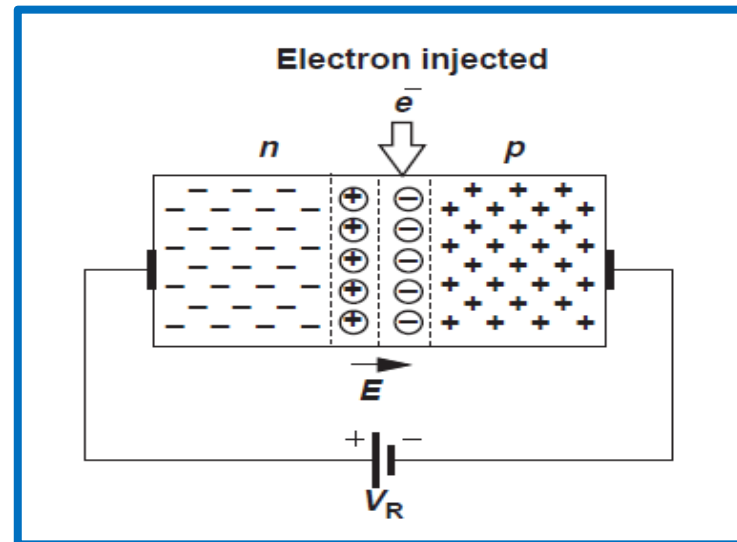
## ❑ Carrier Injection

- ❑ Reverse Biased pn-junction
- ❑ Electrons are injected into the depletion region
- ❑ Experiences E-field in the depletion region
- ❑ Swept away into the n-side of the pn-junction




- ❑ “Reverse biased” pn-junction can efficiently “collect” externally injected electrons



# Physics of Bipolar Junction Transistors

## □ Operation of Bipolar Junction Transistors (BJTs)

### □ Circuit Configurations

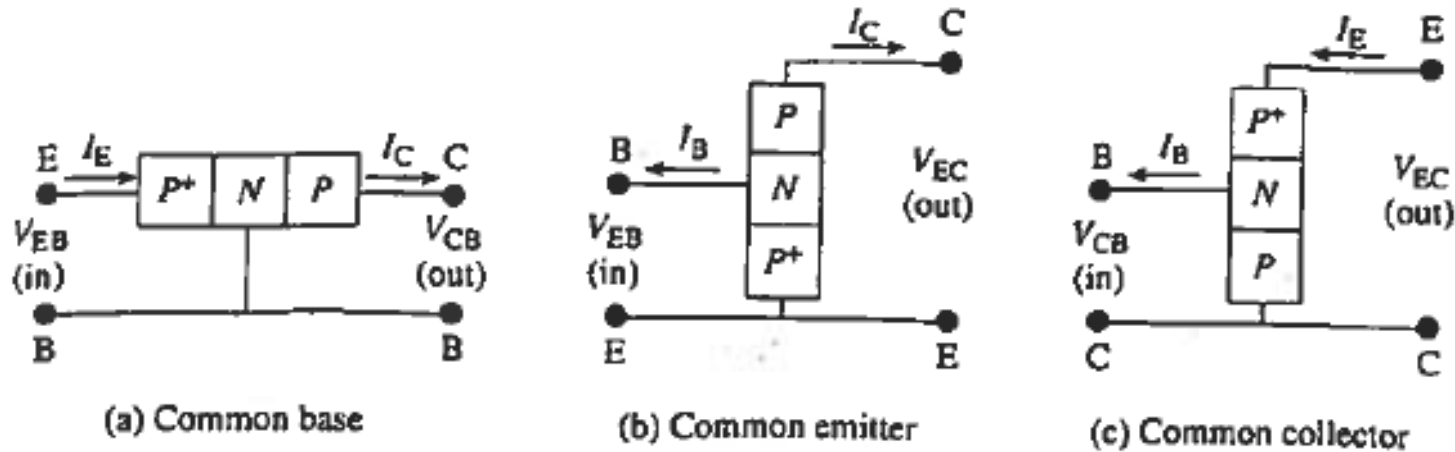

**Figure 10.3** Circuit configurations: (a) common base; (b) common emitter; and (c) common collector.


$$I_E = I_B + I_C$$

$$V_{EB} + V_{BC} + V_{CE} = 0$$

# Physics of Bipolar Junction Transistors

## □ Operation of Bipolar Junction Transistors (BJTs)

### □ Operation / Biasing Modes

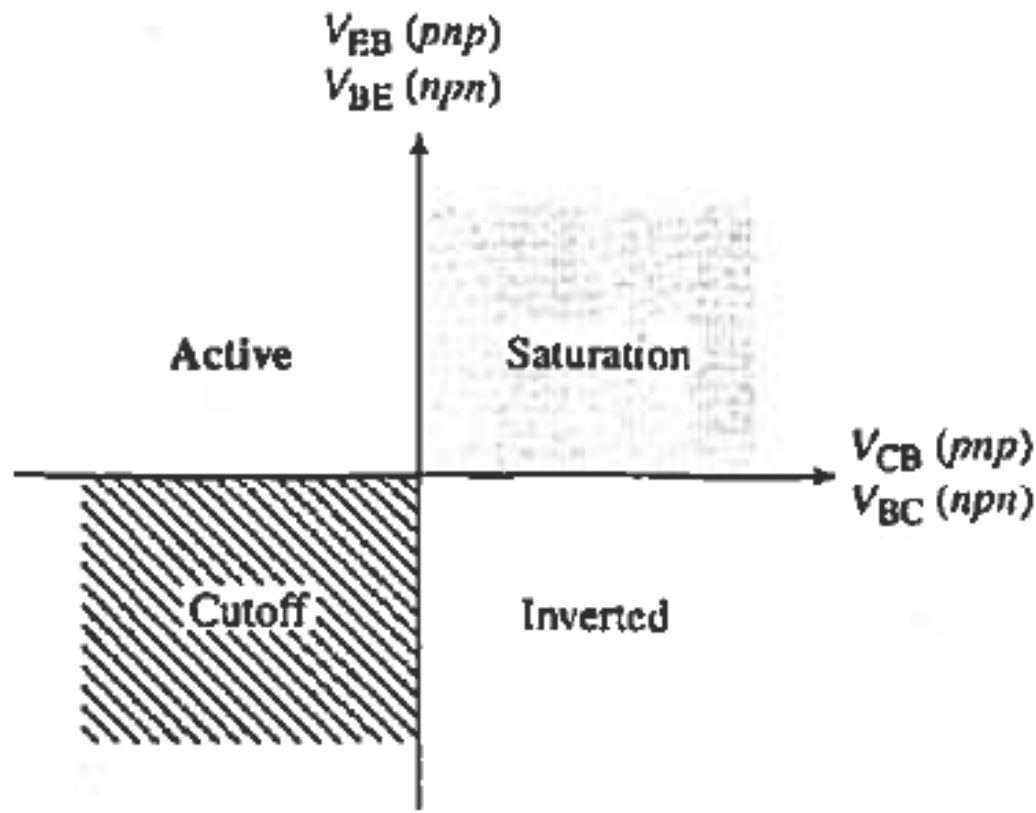

**Table 10.1** Biasing Modes.


<i>Biasing Mode</i>	<i>Biasing Polarity E-B Junction</i>	<i>Biasing Polarity C-B Junction</i>
Saturation	Forward	Forward
Active	Forward	Reverse
Inverted	Reverse	Forward
Cutoff	Reverse	Reverse

# Physics of Bipolar Junction Transistors

## □ Operation of Bipolar Junction Transistors (BJTs)


### □ Output Characteristics
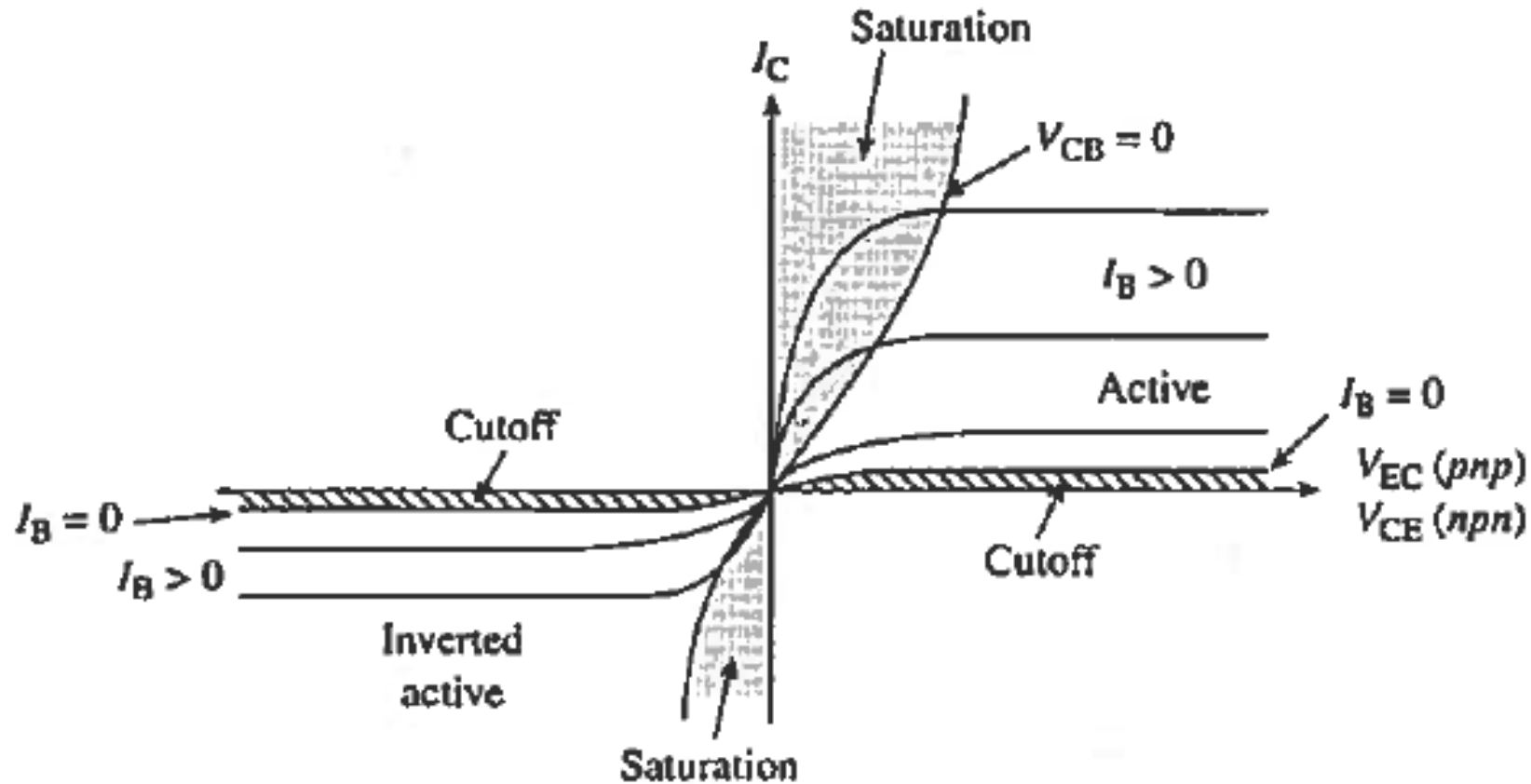
#### □ Common Emitter (CE) Biasing Configuration



# Physics of Bipolar Junction Transistors

## □ Operation of Bipolar Junction Transistors (BJTs)

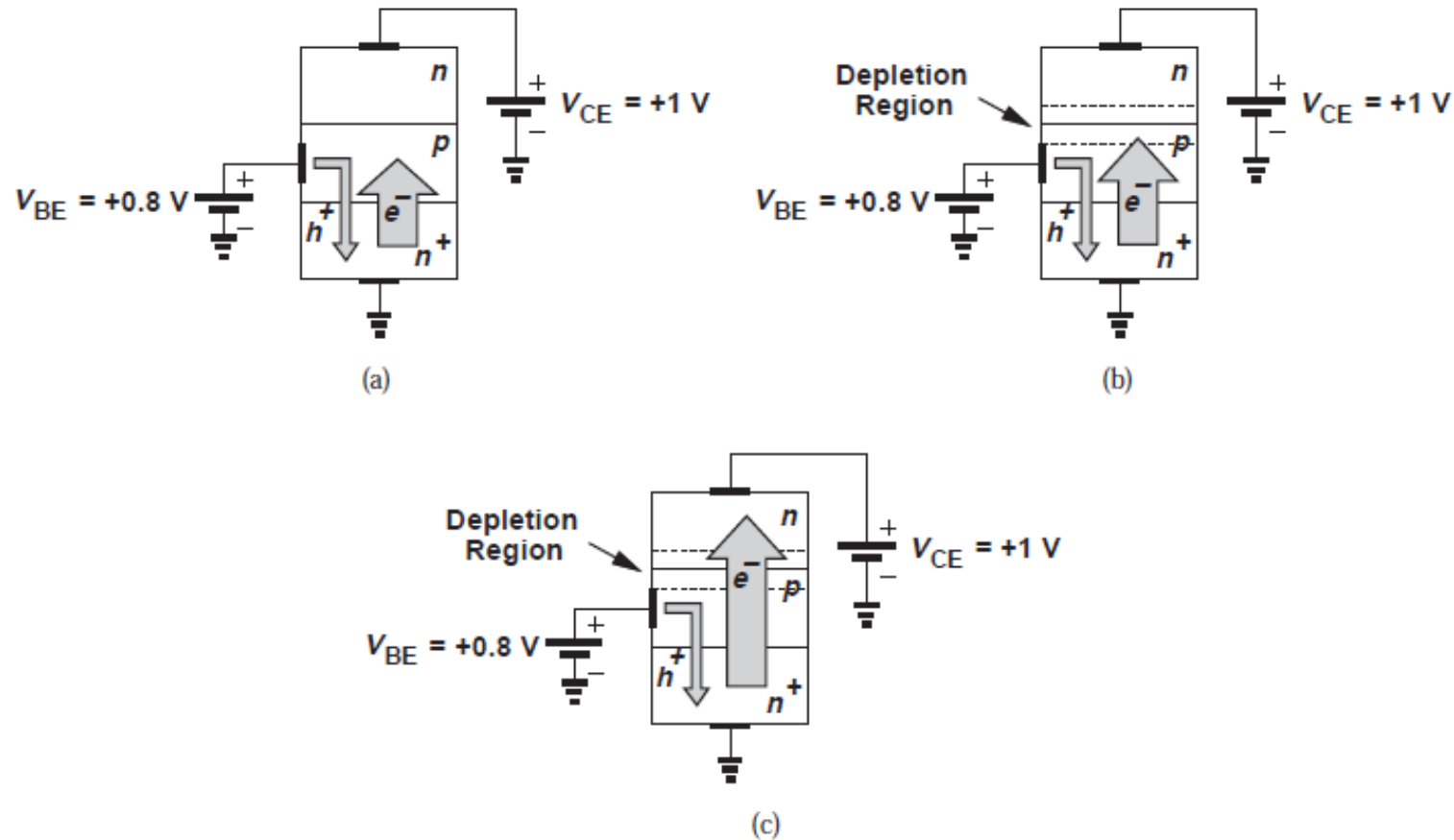

**Figure 4.7** (a) Flow of electrons and holes through base-emitter junction, (b) electrons approaching collector junction, (c) electrons passing through collector junction.

# Physics of Bipolar Junction Transistors

## □ Operation of Bipolar Junction Transistors (BJTs)

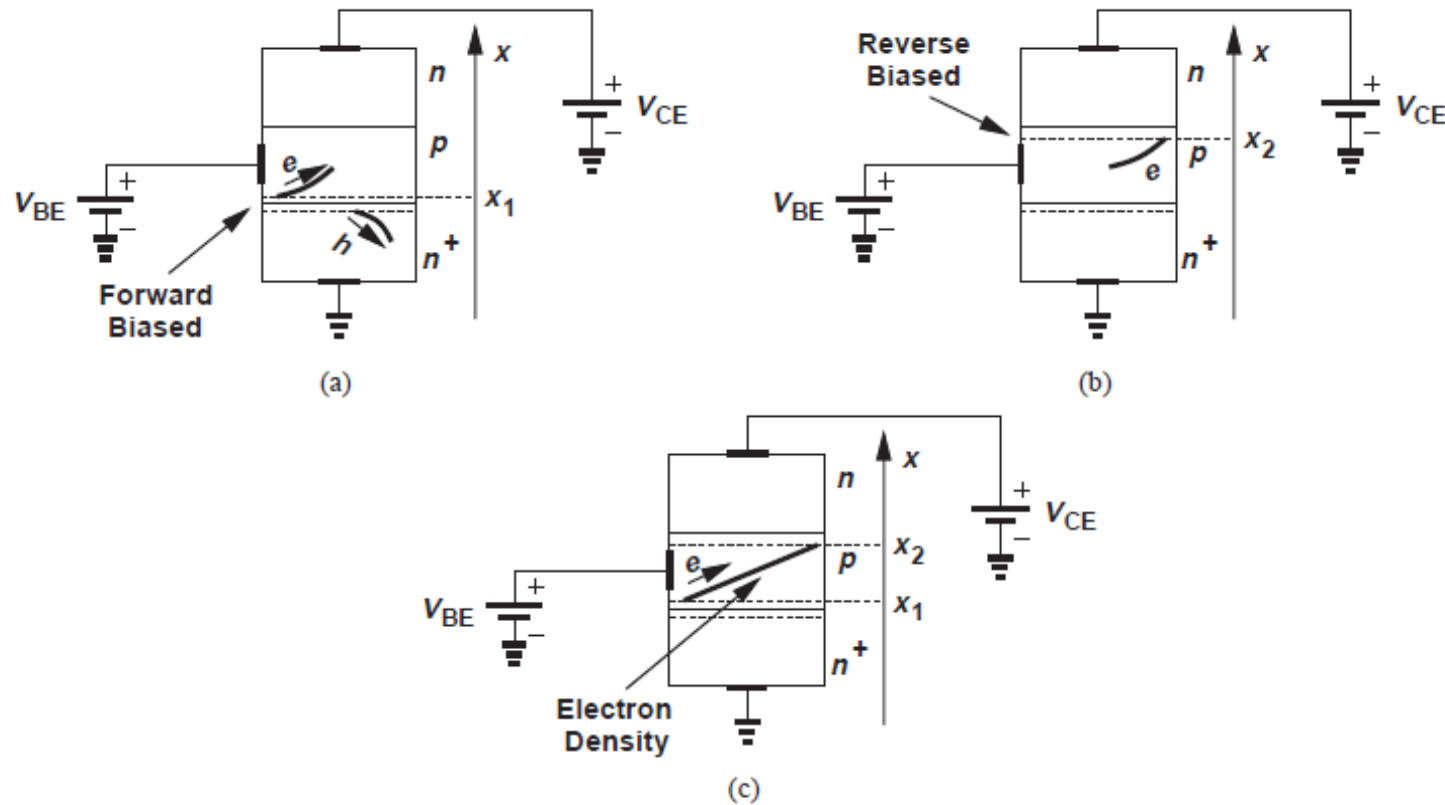


Figure 4.8 (a) Hole and electron profiles at base-emitter junction, (b) zero electron density near collector, (c) electron profile in base.

# Physics of Bipolar Junction Transistors

## ❑ Operation of Bipolar Junction Transistors (BJTs)

### ❑ Collector Current and Terminal Voltages

$$I_C = \frac{A_E q D_n n_i^2}{N_B W_B} \left( \exp \frac{V_{BE}}{V_T} - 1 \right)$$

Collector Current

$$I_C = I_S \exp \frac{V_{BE}}{V_T}$$

Diode Current Equation

❑ Comparing the above equation, we can say that

- In active mode operation, the collector current doesn't depend on collector voltage
- For a fixed  $V_{BE}$ , the device draws a constant current, acting as a current source, provided that  $V_{CE} > V_{BE}$

# Physics of Bipolar Junction Transistors

## ❑ Operation of Bipolar Junction Transistors (BJTs)

### ❑ Collector Current and Terminal Voltages

- BJT operates as voltage-controlled current source (or voltage-dependent current source)
- BJT performs voltage to current conversion
- BJT is a good candidate for amplification

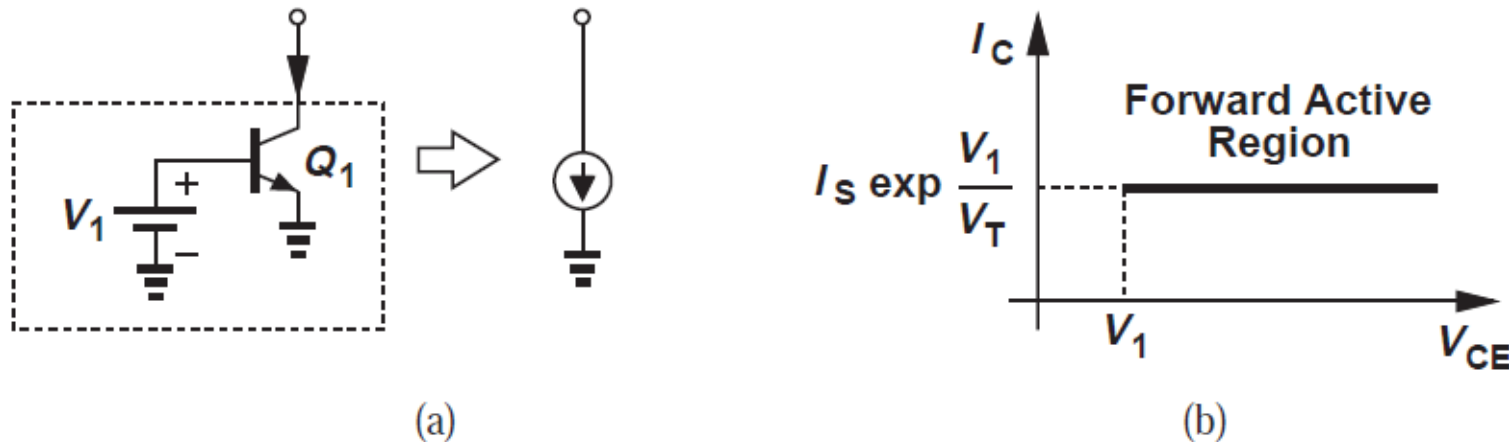


Figure 4.11 (a) Bipolar transistor as a current source, (b) I/V characteristic.

# Physics of Bipolar Junction Transistors

## Example 4.2

Determine the current  $I_X$  in Fig. 4.9(a) if  $Q_1$  and  $Q_2$  are identical and operate in the active mode and  $V_1 = V_2$ .

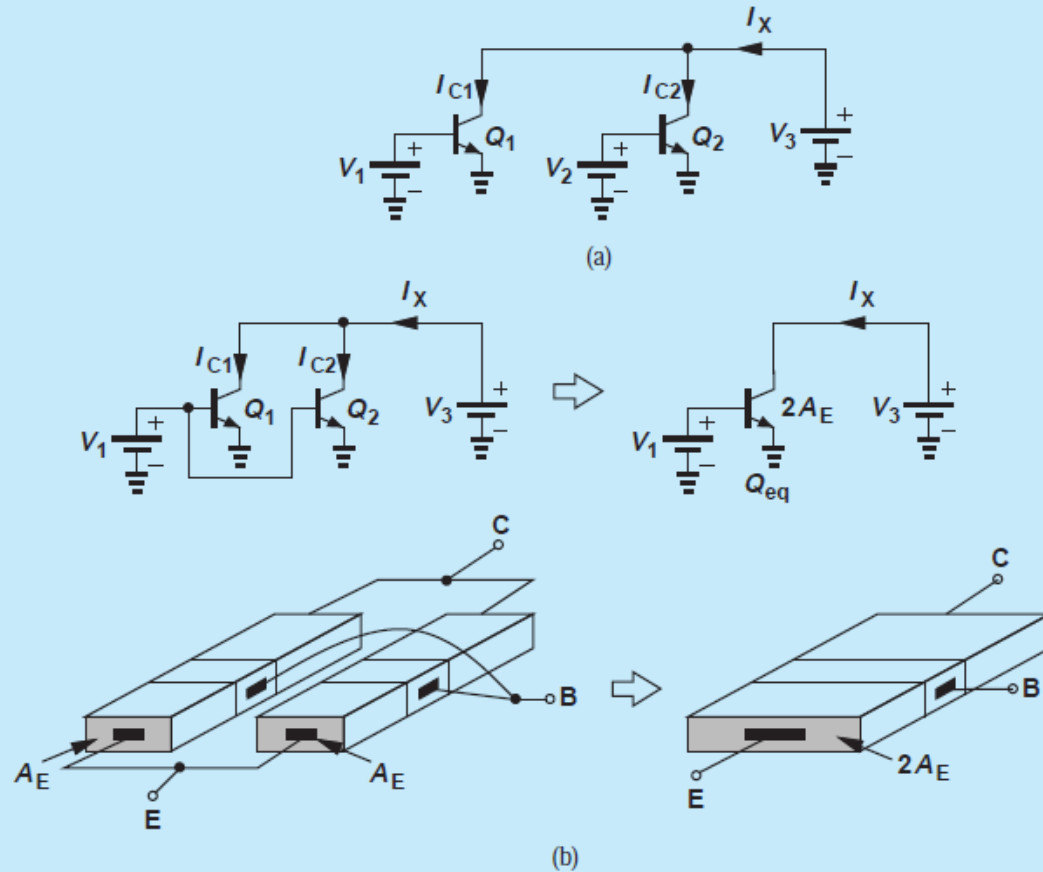


Figure 4.9 (a) Two identical transistors drawing current from  $V_C$ , (b) equivalence to a single transistor having twice the area.

**Remember**

$$I_C = \frac{A_E q D_n n_i^2}{N_B W_B} \left( \exp \frac{V_{BE}}{V_T} - 1 \right)$$



# Physics of Bipolar Junction Transistors

## Example 4.3

In the circuit of Fig. 4.9 (a),  $Q_1$  and  $Q_2$  are identical and operate in the active mode. Determine  $V_1 - V_2$  such that  $I_{C1} = 10I_{C2}$ .

# Physics of Bipolar Junction Transistors

## Example 4.4

Typical discrete bipolar transistors have a large area, e.g.,  $500\ \mu\text{m} \times 500\ \mu\text{m}$ , whereas modern integrated devices may have an area as small as  $0.5\ \mu\text{m} \times 0.2\ \mu\text{m}$ . Assuming other device parameters are identical, determine the difference between the base-emitter voltage of two such transistors for equal collector currents.

# Physics of Bipolar Junction Transistors

## Example 4.5

Determine the output voltage in Fig. 4.10 if  $I_S = 5 \times 10^{-16}$  A.

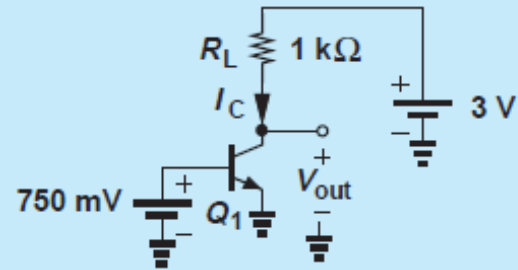


Figure 4.10 Simple stage with biasing.

# Physics of Bipolar Junction Transistors

## □ Base and Emitter Currents

□  $\beta$  is the current gain of the BJT transistor

□ BJT equations are given below

$$I_C = I_S \exp \frac{V_{BE}}{V_T}$$

$$I_E = I_C + I_B$$

$$I_C = \beta I_B$$

$$\begin{aligned} I_E &= I_C + I_B \\ &= I_C \left( 1 + \frac{1}{\beta} \right) \end{aligned}$$

$$\begin{aligned} I_C &= I_S \exp \frac{V_{BE}}{V_T} \\ I_B &= \frac{1}{\beta} I_S \exp \frac{V_{BE}}{V_T} \\ I_E &= \frac{\beta + 1}{\beta} I_S \exp \frac{V_{BE}}{V_T} \end{aligned}$$

# Physics of Bipolar Junction Transistors


## ❑ Large-Signal Model

- ❑ Some textbooks consider this as DC – model
- ❑ Large signal model is concerned with the biasing of the circuit with effort to make sure the BJT remains in its desired mode of operation e.g., Forward Active mode
- ❑ The voltages and current applied are considerably of large values making sure the BJT remains in its desired mode of operation

# Physics of Bipolar Junction Transistors

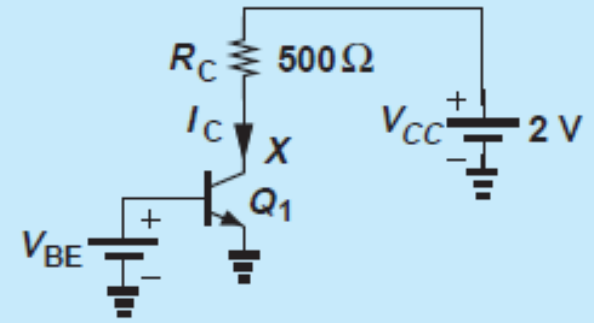
## Example 4.7

Consider the circuit shown in Fig. 4.14 (a), where  $I_{S,Q1} = 5 \times 10^{-17} \text{ A}$  and  $V_{BE} = 800 \text{ mV}$ . Assume  $\beta = 100$ . (a) Determine the transistor terminal currents and voltages and verify that the device indeed operates in the active mode. (b) Determine the maximum value of  $R_C$  that permits operation in the active mode.



# Physics of Bipolar Junction Transistors

## □ I-V Characteristics

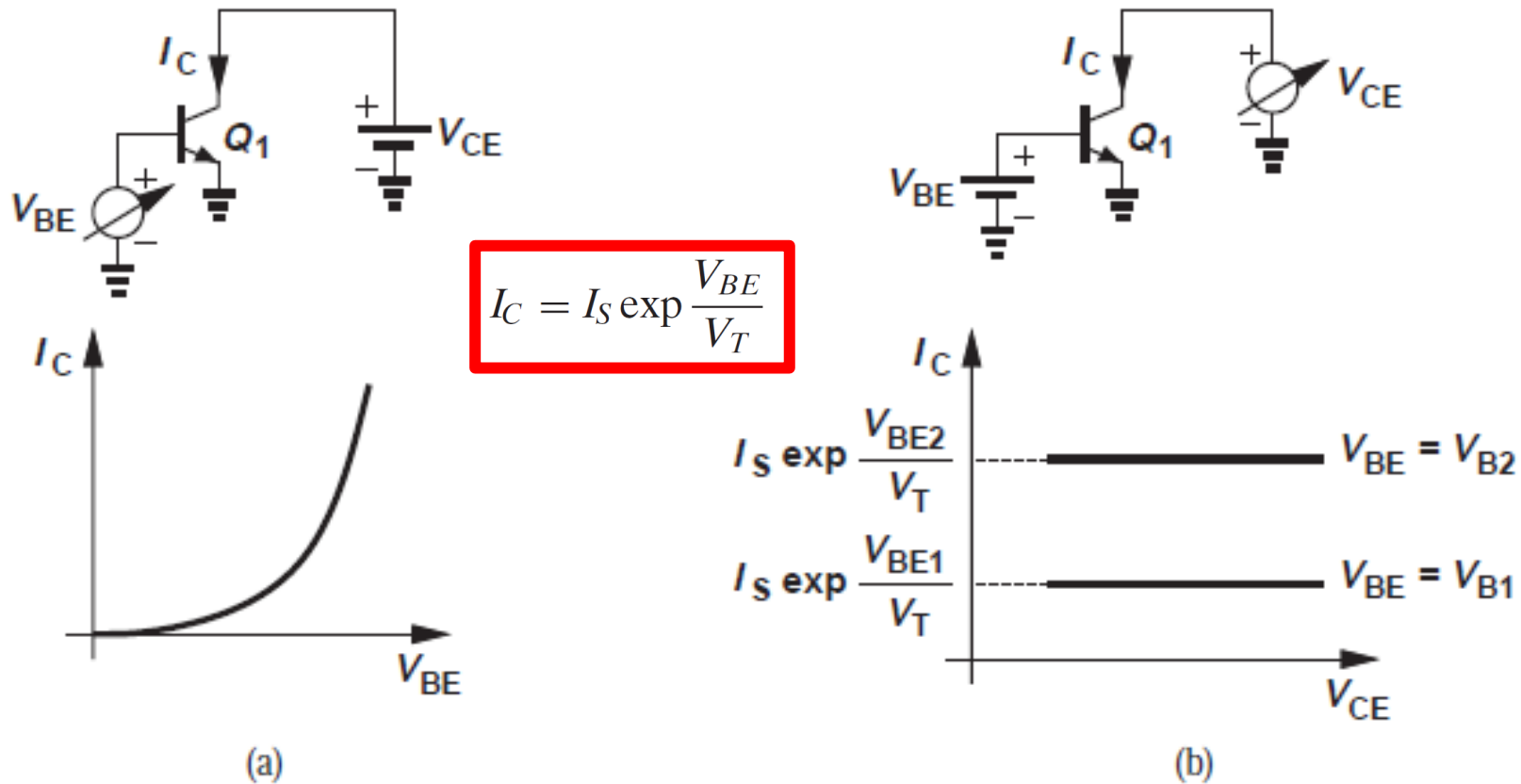


**Figure 4.15** Collector current as a function of (a) base-emitter voltage and (b) collector-emitter voltage.

# Physics of Bipolar Junction Transistors

## Example 4.8

For a bipolar transistor,  $I_S = 5 \times 10^{-17}$  A and  $\beta = 100$ . Construct the  $I_C$ - $V_{BE}$ ,  $I_C$ - $V_{CE}$ ,  $I_B$ - $V_{BE}$ , and  $I_B$ - $V_{CE}$  characteristics.

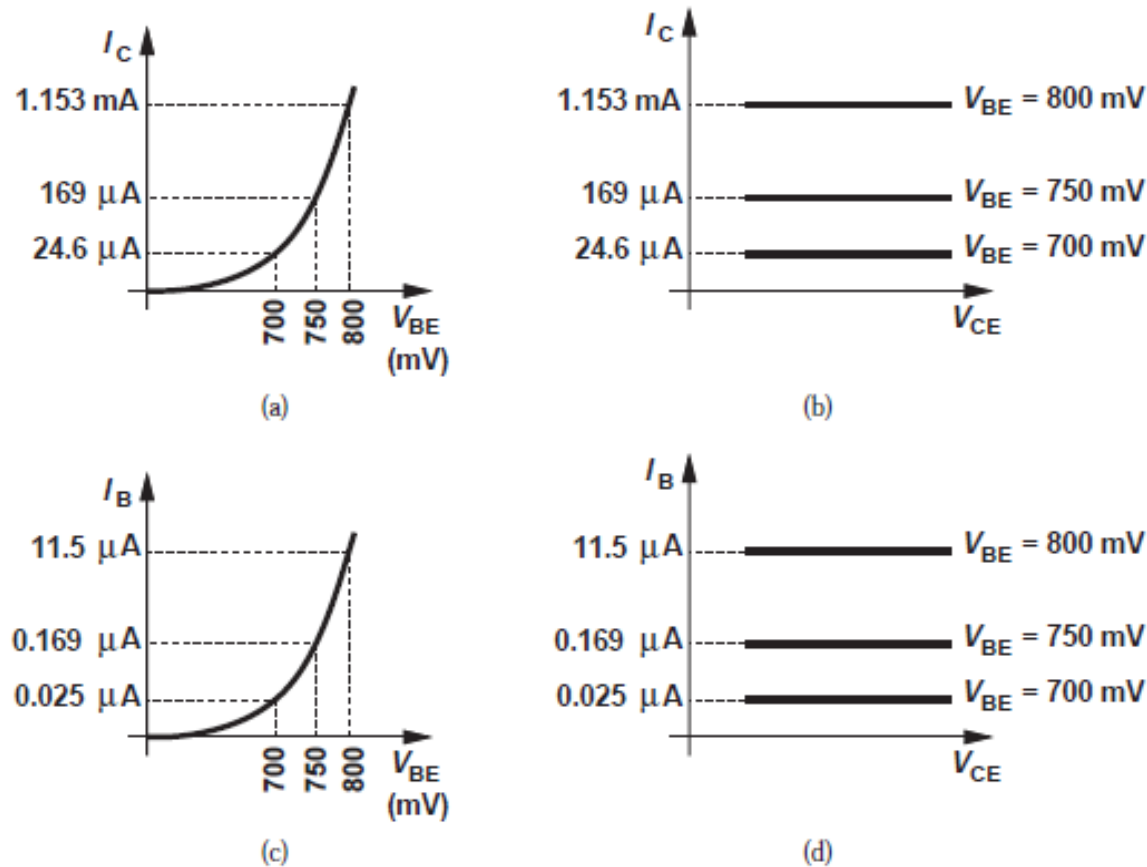

**Figure 4.16** (a) Collector current as a function of  $V_{BE}$ , (b) collector current as a function of  $V_{CE}$ , (c) base current as a function of  $V_{BE}$ , (d) base current as a function of  $V_{CE}$ .



# Physics of Bipolar Junction Transistors



## □ Transconductance

$$g_m = \frac{dI_C}{dV_{BE}}$$

$$g_m = \frac{d}{dV_{BE}} \left( I_S \exp \frac{V_{BE}}{V_T} \right)$$

$$= \frac{1}{V_T} I_S \exp \frac{V_{BE}}{V_T}$$


$$= \frac{I_C}{V_T}$$

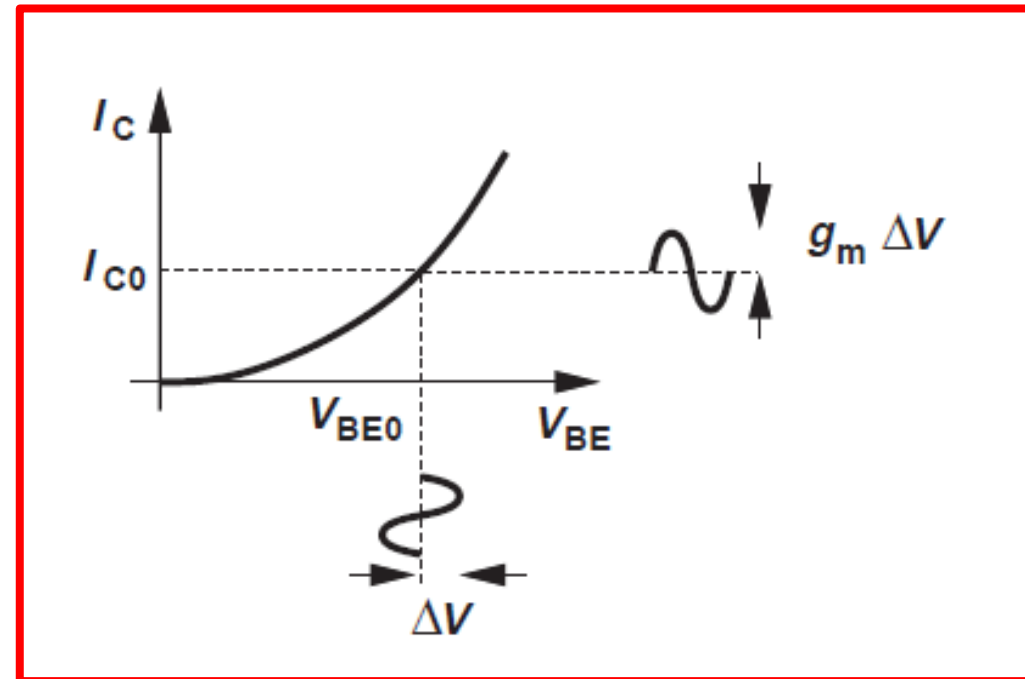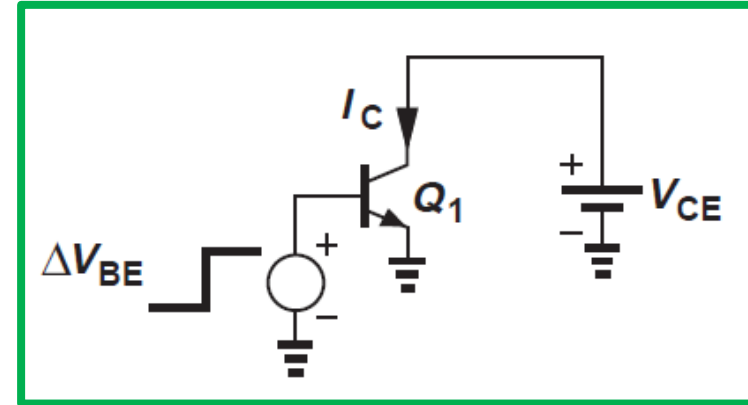

# Physics of Bipolar Junction Transistors

## □ Transconductance
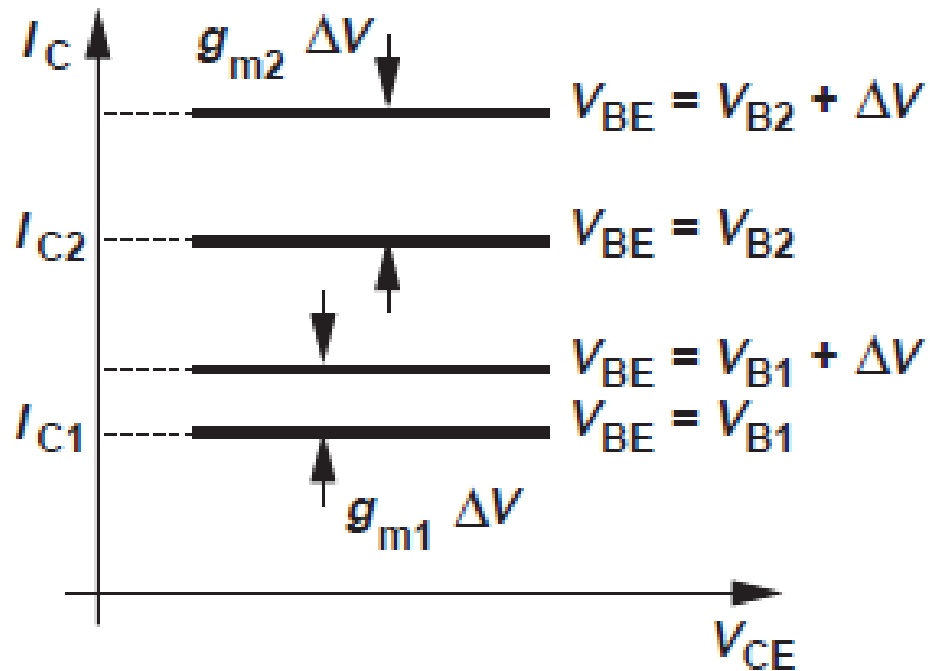
### □ Transconductance for different collector bias currents



$$g_m = \frac{I_C}{V_T}$$

$$g_m = \frac{dI_C}{dV_{BE}}$$

$$I_C = I_S \exp \frac{V_{BE}}{V_T}$$

- Two different bias currents  $I_{C1}$  and  $I_{C2}$ , the plots reveal that a change of  $\Delta V$  in  $V_{BE}$  results in a greater change in  $I_C$  for operation around  $I_{C2}$  than around  $I_{C1}$  because  $g_{m2} > g_{m1}$

# Physics of Bipolar Junction Transistors

## □ Transconductance

□ The BJT acts as a voltage-dependent current source when operating in the forward active region

### □ What is the measure of goodness of a voltage-dependent current source ?

□ Voltage-to-Current conversion property of a transistor (particularly for amplification of signals)

□ We ask ourselves – “If the input signal voltage at the base-emitter changes, how much change is produced in the collector current ?”

□ Basically, we are concerned with  $\Delta I_C / \Delta V_{BE}$ . This ratio is called “transconductance,  $g_m$ ”

□ Much similar to small signal resistance of diodes

$$g_m = \frac{dI_C}{dV_{BE}}.$$

# Physics of Bipolar Junction Transistors

## □ Transconductance

□ The transconductance is fundamentally a function of the collector current rather than the base current

### □ For example:


✓ If  $I_C$  remains constant but  $\beta$  varies, then  $g_m$  does not change but  $I_B$  does

□ For this reason, the collector bias current plays a central role in the analysis and design, with the base current viewed as secondary, often undesirable effect

# Physics of Bipolar Junction Transistors

## □ Small-Signal Modeling

- Remember the small-signal modeling help us to analyze the transistors in a linear fashion
- Consider two cases
  - Excitation (perturbation) at base-emitter terminal (from the input side)
  - Excitation (perturbation) at collector-emitter terminal (from the output side)

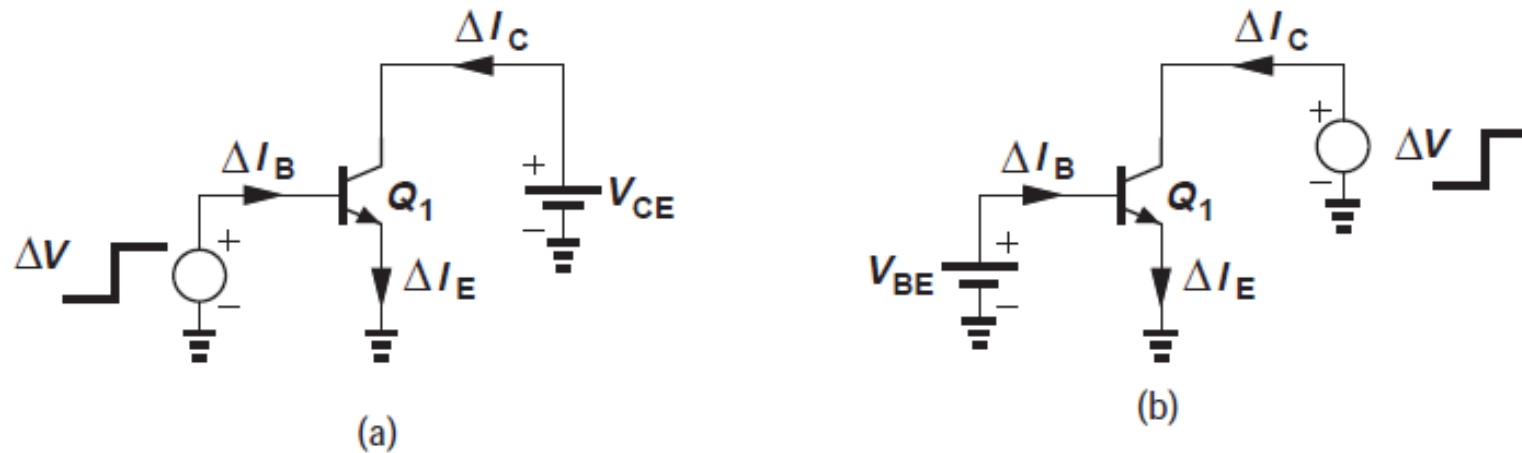

**Figure 4.21** Excitation of bipolar transistor with small changes in (a) base-emitter and (b) collector-emitter voltage.

# Physics of Bipolar Junction Transistors

## □ Small-Signal Modeling

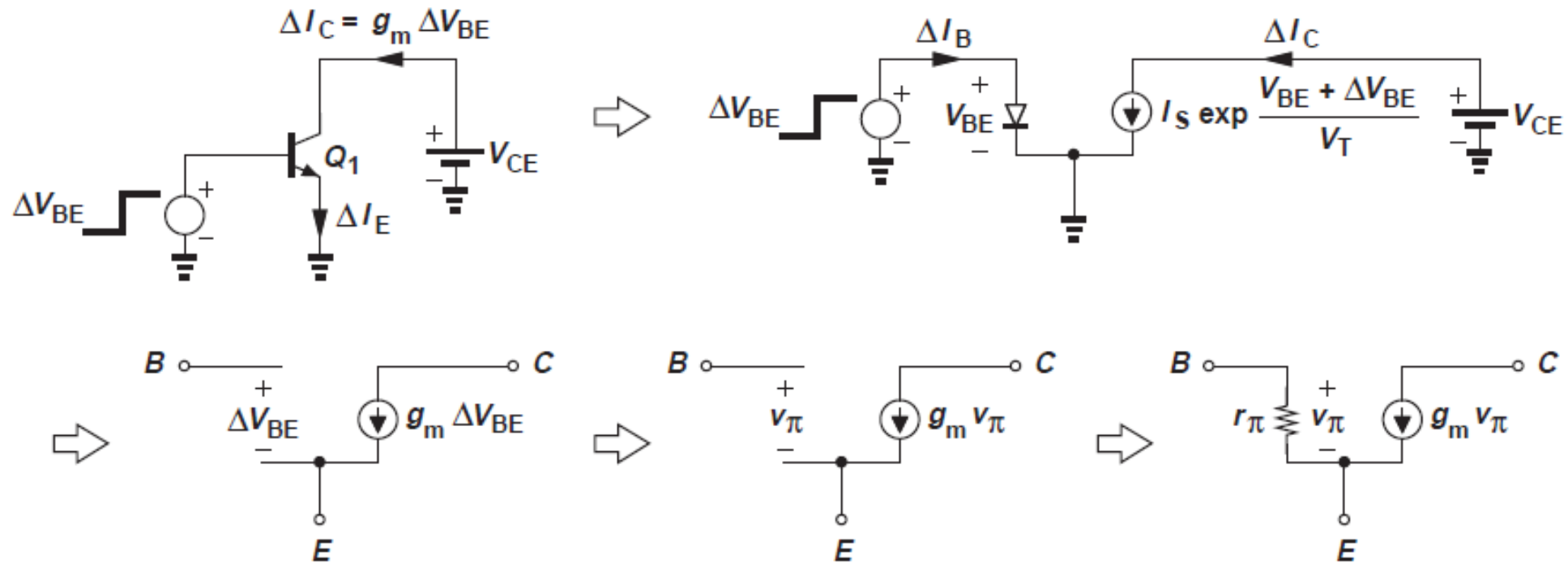


Figure 4.22 Development of small-signal model.

# Physics of Bipolar Junction Transistors

## □ Small-Signal Modeling

□ We know that

$$\Delta I_C = g_m \Delta V_{BE}$$

□ The change in  $V_{BE}$  creates a change in  $I_C$  but also creates a change in  $I_B$

$$\begin{aligned}\Delta I_B &= \frac{\Delta I_C}{\beta} \\ &= \frac{g_m}{\beta} \Delta V_{BE}\end{aligned}$$

□ The resistance between the base-emitter terminals is given by  $r_\pi$

$$\begin{aligned}r_\pi &= \frac{\Delta V_{BE}}{\Delta I_B} \\ &= \frac{\beta}{g_m}.\end{aligned}$$

# Physics of Bipolar Junction Transistors

## □ Small-Signal Modeling


- This shows that the forward-biased diode between the base and the emitter is modeled by a small-signal resistance equal to  $\beta/g_m$
- This result is expected because the diode carries a bias current equal to  $I_C / \beta$  and exhibits a small-signal resistance of  $V_T / (I_C/\beta) = \beta (V_T/I_C) = \beta/g_m$



# Physics of Bipolar Junction Transistors
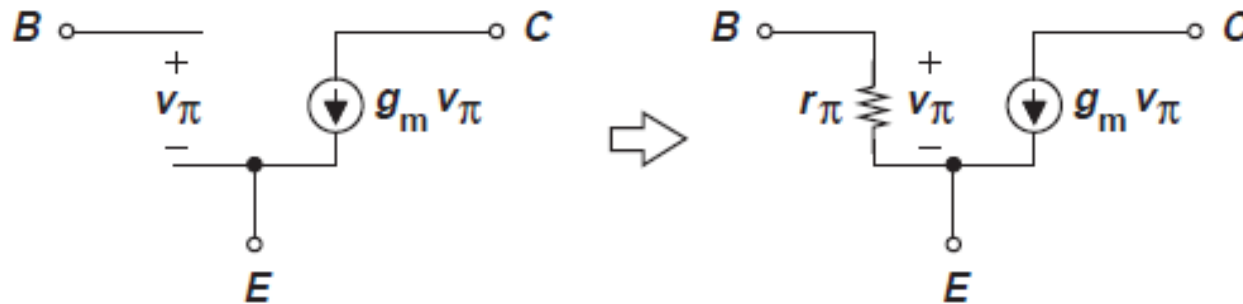
## □ Small-Signal Modeling


- We now turn our attention to the collector and apply a voltage change with respect to the emitter i.e., from the output side
- For a constant  $V_{BE}$ , the collector voltage has no effect on  $I_C$  or  $I_B$  because  $I_C = I_S \exp(V_{BE}/V_T)$  and  $I_B = I_C / \beta$
- Since  $\Delta V_{CE}$  leads to no change in any of the terminal currents, the model developed need not be altered



# Physics of Bipolar Junction Transistors
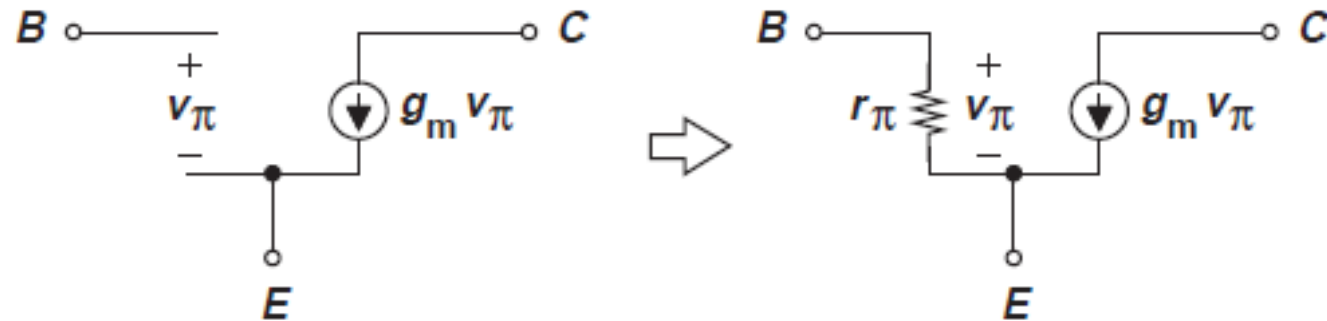
## □ Small-Signal Modeling


- Both parameters of the model,  $g_m$  and  $r_\pi$ , depend on the bias current of the device
- With a high collector bias current, a greater  $g_m$  is obtained, but the impedance between the base and emitter falls to lower values



# Physics of Bipolar Junction Transistors
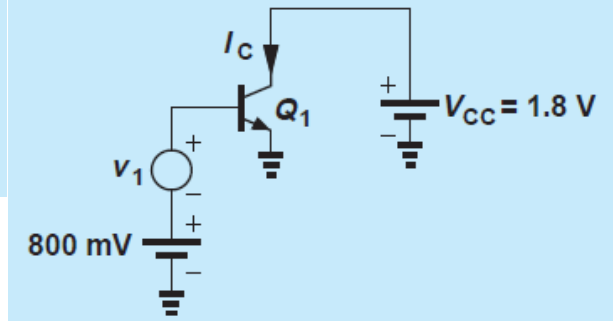
## Example 4.10


Consider the circuit shown in Fig. 4.24(a), where  $v_1$  represents the signal generated by a microphone,  $I_S = 3 \times 10^{-16} \text{ A}$ ,  $\beta = 100$ , and  $Q_1$  operates in the active mode. (a) If  $v_1 = 0$ , determine the small-signal parameters of  $Q_1$ . (b) If the microphone generates a 1-mV signal, how much change is observed in the collector and base currents?



# Physics of Bipolar Junction Transistors
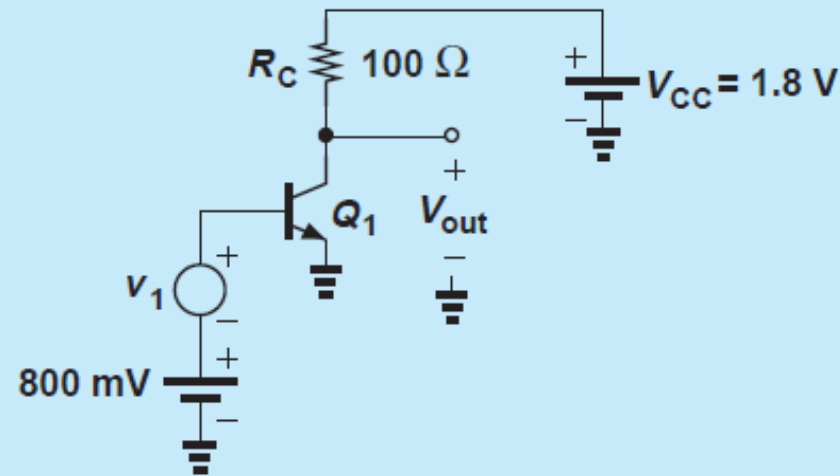
## Example 4.11

The circuit of Fig. 4.24 (a) is modified as shown in Fig. 4.25, where resistor  $R_C$  converts the collector current to a voltage. (a) Verify that the transistor operates in the active mode. (b) Determine the output signal level if the microphone produces a 1-mV signal.



# Physics of Bipolar Junction Transistors


## Example 4.12

Considering the circuit of Example 4.11, suppose we raise  $R_C$  to  $200\ \Omega$  and  $V_{CC}$  to  $3.6\text{ V}$ . Verify that the device operates in the active mode and compute the voltage gain.

# Physics of Bipolar Junction Transistors

## □ Early Effect

- We have to incorporate the second order effects in our modeling to achieve a more realistic analysis
- Early Effect is one of such effects that allows us to realize the practical picture of BJT amplifiers where the gain of the devices is “limited” instead of “infinite”

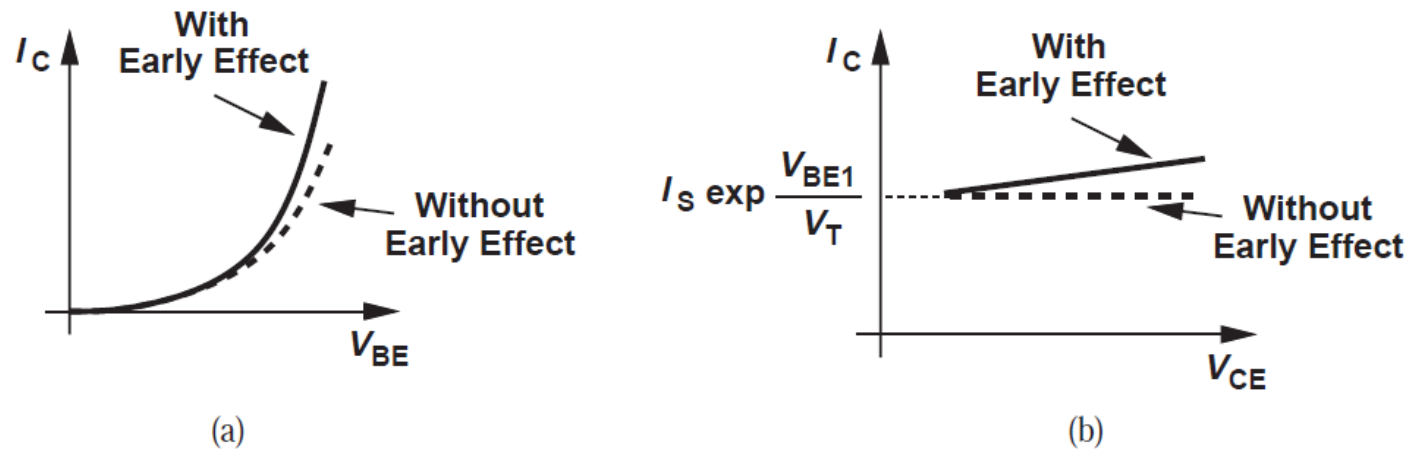


**Figure 4.28** Collector current as a function of (a)  $V_{BE}$  and (b)  $V_{CE}$  with and without Early effect.

$$I_C = \frac{A_E q D_n n_i^2}{N_E W_B} \left( \exp \frac{V_{BE}}{V_T} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right),$$
$$\approx \left( I_S \exp \frac{V_{BE}}{V_T} \right) \left( 1 + \frac{V_{CE}}{V_A} \right).$$

# Physics of Bipolar Junction Transistors
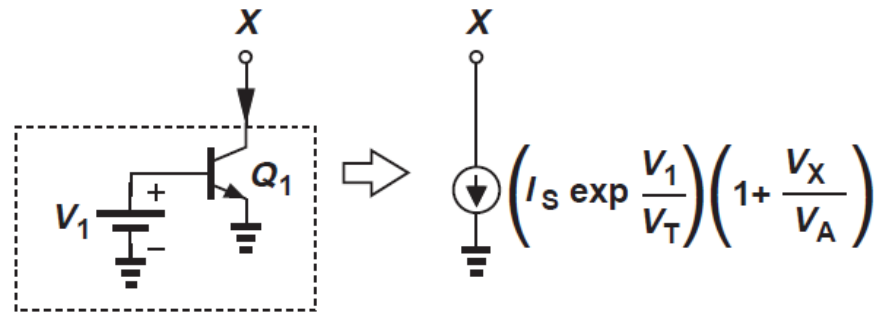
## □ Early Effect

- The  $I_C - V_{CE}$  curves show that the BJT transistor does not behave as a constant current source
- The transistor can still be viewed as a two-terminal device but with a current that varies to some extent with  $V_{CE}$



$$I_C = \frac{A_E q D_n n_i^2}{N_E W_B} \left( \exp \frac{V_{BE}}{V_T} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right),$$
$$\approx \left( I_S \exp \frac{V_{BE}}{V_T} \right) \left( 1 + \frac{V_{CE}}{V_A} \right).$$

Figure 4.29 Realistic model of bipolar transistor as a current source.

# Physics of Bipolar Junction Transistors

## □ Early Effect – Large Signal Model

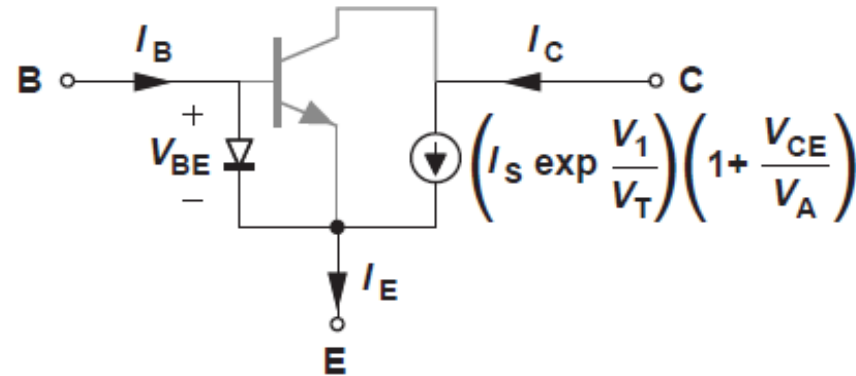


Figure 4.30 Large-signal model of bipolar transistor including Early effect.

$$I_C = \left(I_S \exp \frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$I_B = \frac{1}{\beta} \left(I_S \exp \frac{V_{BE}}{V_T}\right)$$

$$I_E = I_C + I_B.$$



# Physics of Bipolar Junction Transistors

## □ Early Effect – Small Signal Model

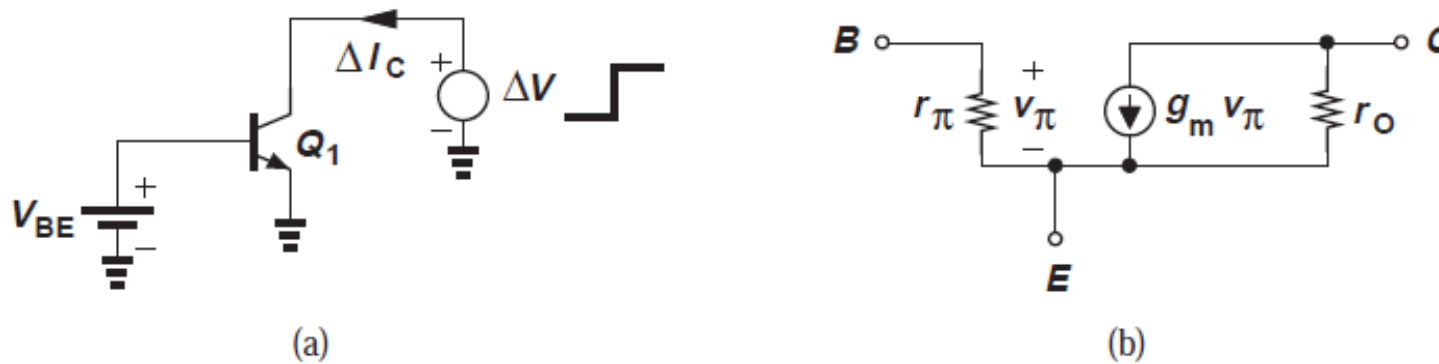


Figure 4.31 (a) Small change in  $V_{CE}$  and (b) small-signal model including Early effect.

$$\begin{aligned} r_o &= \frac{\Delta V_{CE}}{\Delta I_C} \\ &= \frac{V_A}{I_S \exp \frac{V_{BE}}{V_T}} \\ &\approx \frac{V_A}{I_C}. \end{aligned}$$

# Physics of Bipolar Junction Transistors

## □ Early Effect – Small Signal Model

### Example 4.14


A transistor is biased at a collector current of 1 mA. Determine the small-signal model if  $\beta = 100$  and  $V_A = 15$  V.

# Physics of Bipolar Junction Transistors
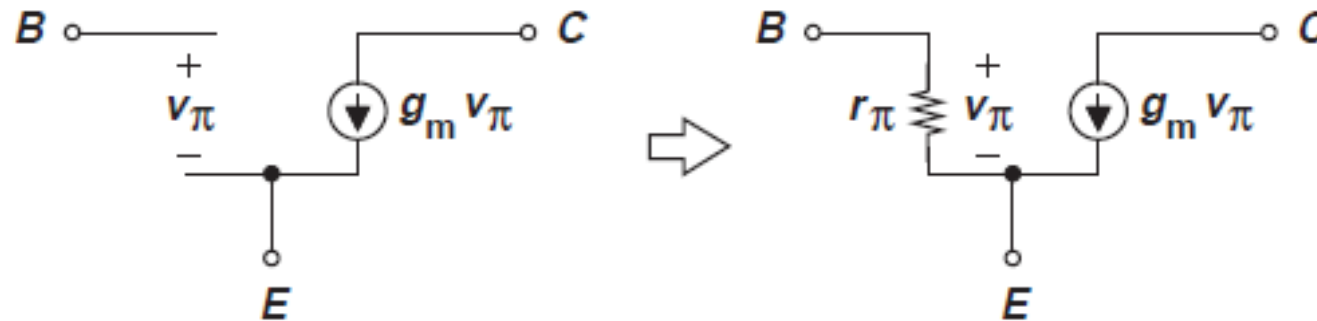
## □ Small-Signal Modeling

□ Both parameters of the model,  $g_m$  and  $r_\pi$ , depend on the bias current of the device

□ With a high collector bias current, a greater  $g_m$  is obtained, but the impedance between the base and emitter falls to lower values



$$\Delta I_C = g_m \Delta V_{BE}$$

$$\begin{aligned}\Delta I_B &= \frac{\Delta I_C}{\beta} \\ &= \frac{g_m}{\beta} \Delta V_{BE}\end{aligned}$$

$$\begin{aligned}r_\pi &= \frac{\Delta V_{BE}}{\Delta I_B} \\ &= \frac{\beta}{g_m}\end{aligned}$$

# Physics of Bipolar Junction Transistors

## □BJT Operation in Saturation Mode

### Example 4.16

For the circuit of Fig. 4.36, determine the relationship between  $R_C$  and  $V_{CC}$  that guarantees operation in soft saturation or active region.


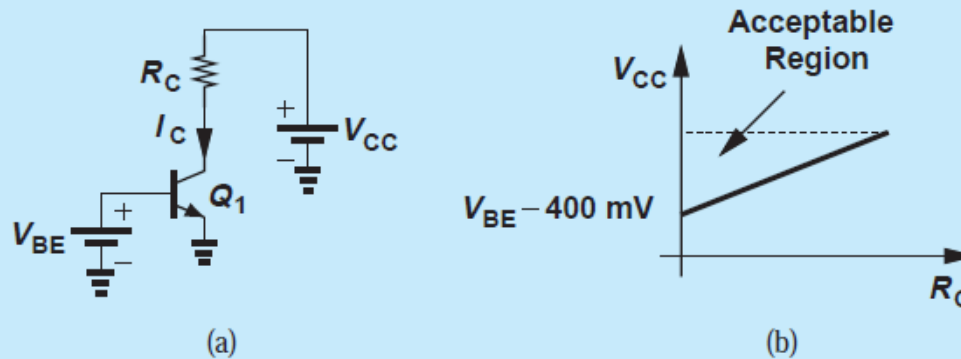


Figure 4.36 (a) Simple stage, (b) acceptable range of  $V_{CC}$  and  $R_C$ .

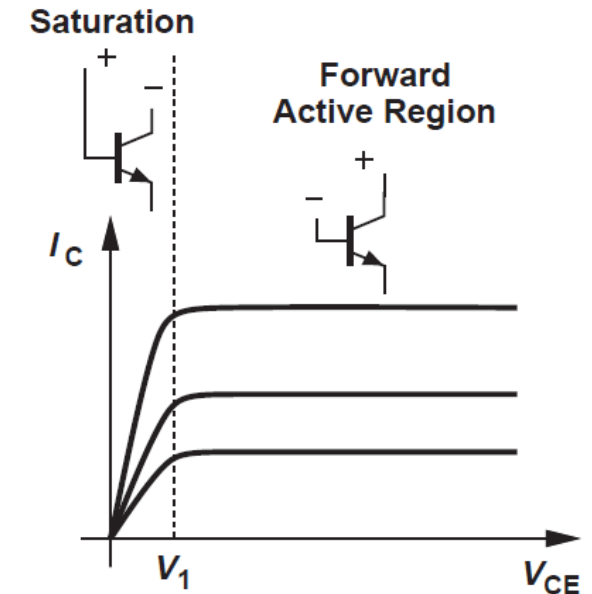

# Chapter – 5

## Bipolar Amplifiers

# Bipolar Amplifiers

## □ Input – Output Impedance of Amplifiers

### □ Ideal Case

- Input Impedance should be infinite
- Output Impedance should be zero

### □ Practical Case


- Input Impedance should be maximized while design
- Output Impedance should be minimized while design

# Bipolar Amplifiers

## □ Input – Output Impedance of Amplifiers


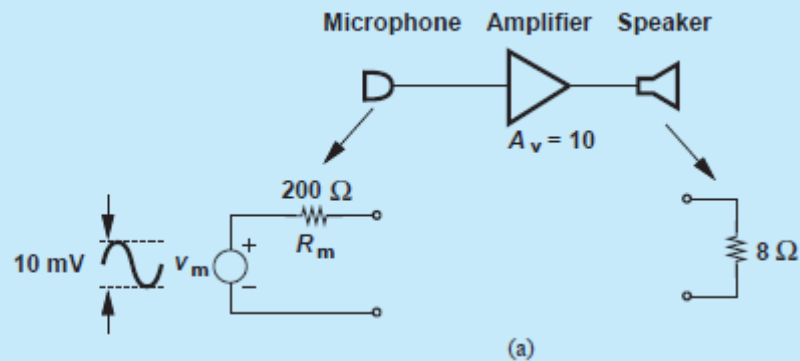
### Example 5.1

An amplifier with a voltage gain of 10 senses a signal generated by a microphone and applies the amplified output to a speaker [Fig. 5.1(a)]. Assume the microphone can be modeled with a voltage source having a 10-mV peak-to-peak signal and a series resistance of  $200\ \Omega$ . Also assume the speaker can be represented by an  $8\text{-}\Omega$  resistor.



(a) Determine the signal level sensed by the amplifier if the circuit has an input impedance of  $2\text{ k}\Omega$  or  $500\ \Omega$ .

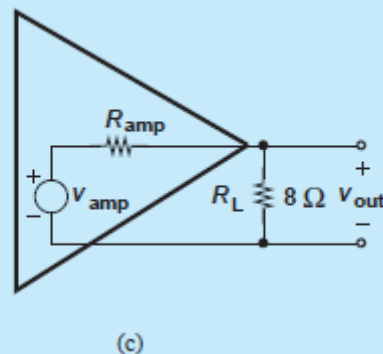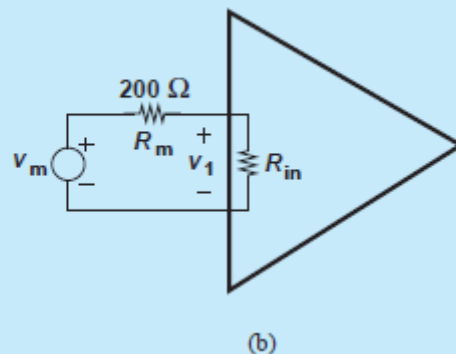
(b) Determine the signal level delivered to the speaker if the circuit has an output impedance of  $10\ \Omega$  or  $2\ \Omega$ .




# Bipolar Amplifiers
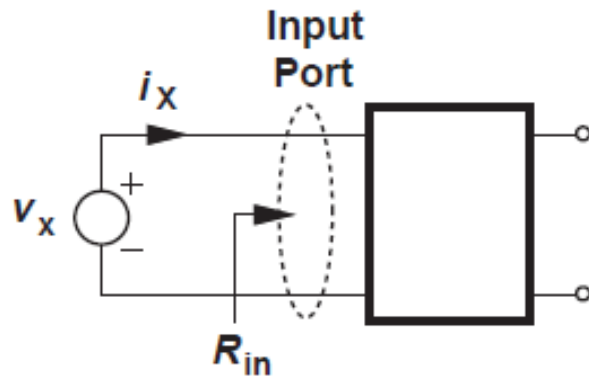
## □ Measurement of Input – Output Impedance

□ Remember the Thevenin's Theorem for finding the impedance



(a)

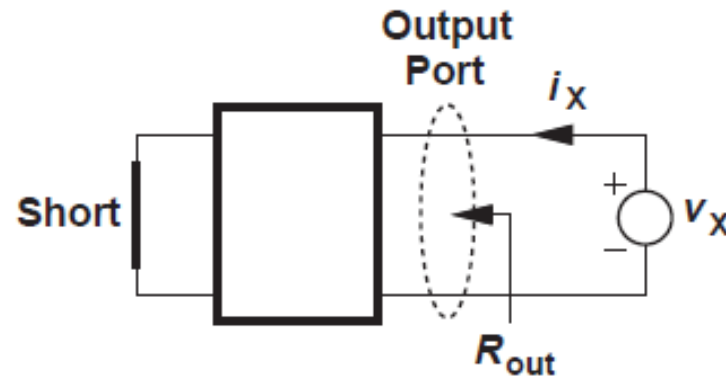

(b)

Measurement of (a) input and (b) output impedances.





# Bipolar Amplifiers

## □ Calculation of Input – Output Impedance
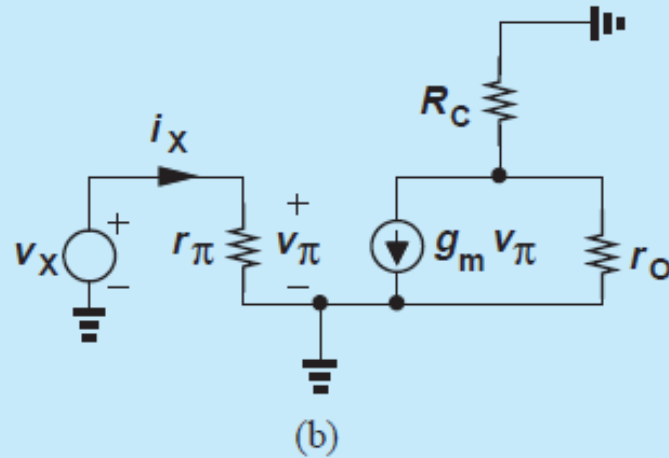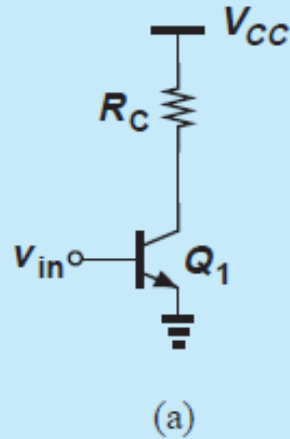
### Example 5.2

Assuming that the transistor operates in the forward active region, determine the input impedance of the circuit shown in Fig. 5.3(a).



**Question:** What happens when  $R_C$  is doubled ?

# Bipolar Amplifiers

## □ Calculation of Input – Output Impedance

### Example 5.3

Calculate the impedance seen looking into the collector of  $Q_1$  in Fig. 5.5(a).

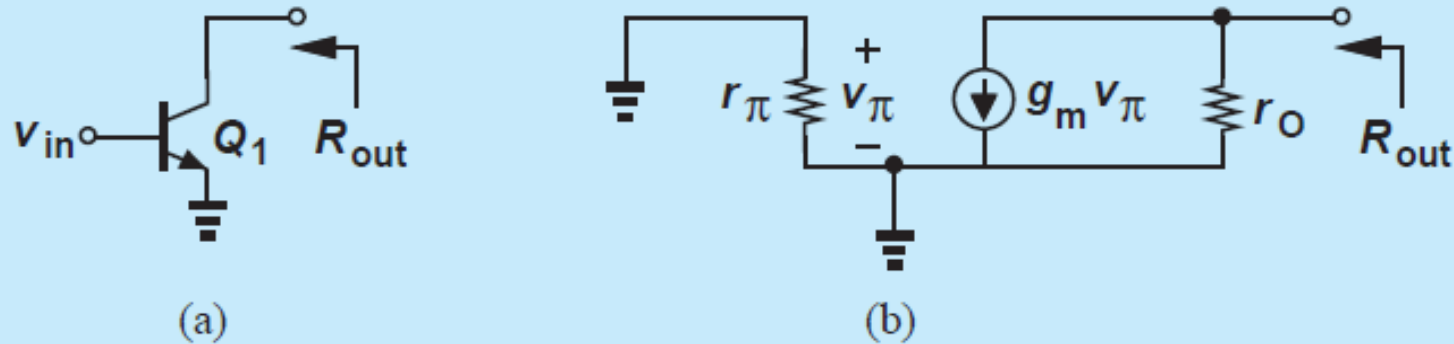


Figure 5.5 (a) Impedance seen at collector, (b) small-signal model.

# Bipolar Amplifiers

## □ Calculation of Input – Output Impedance

### Example 5.4

Calculate the impedance seen at the emitter of  $Q_1$  in Fig. 5.6(a). Neglect the Early effect for simplicity.


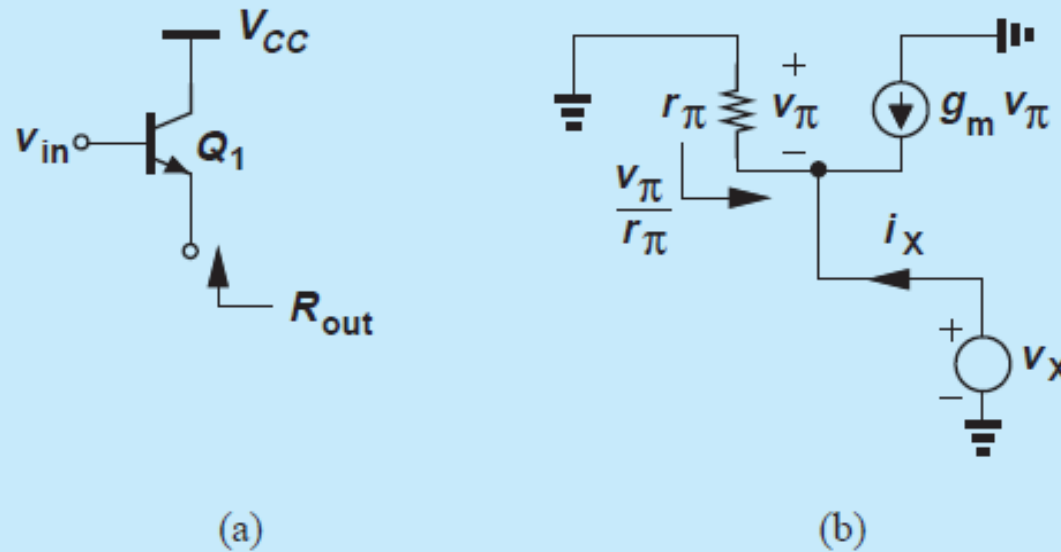


Figure 5.6 (a) Impedance seen at emitter, (b) small-signal model.

# Bipolar Amplifiers
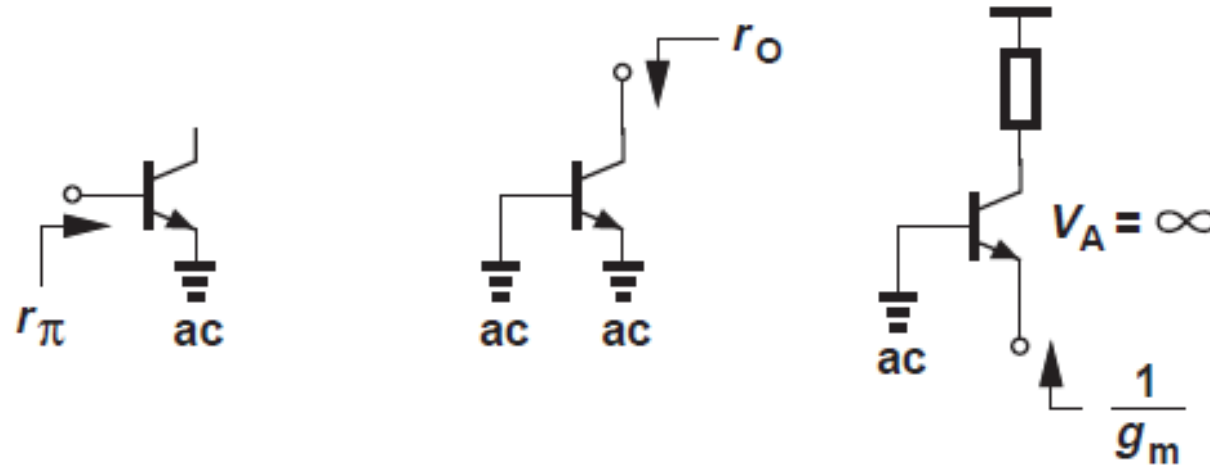
## □Summary – Calculation of Input – Output Impedance




Summary of impedances seen at terminals of a transistor.

# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage

#### □ Case – 1 – Simple Biasing

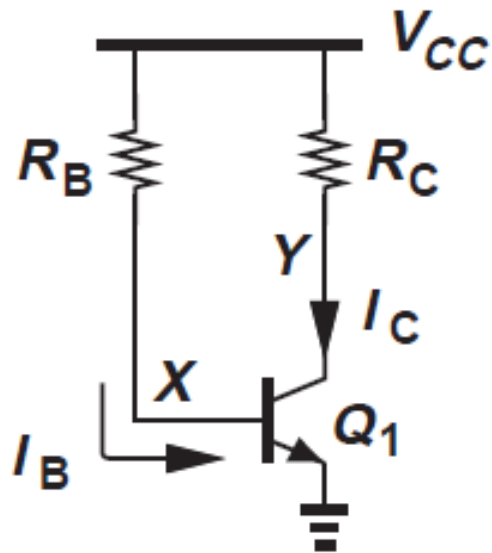

#### Large Signal Analysis (DC – Analysis)

$$R_B I_B + V_{BE} = V_{CC}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}.$$

$$I_C = \beta \frac{V_{CC} - V_{BE}}{R_B},$$

$$\begin{aligned} V_{CE} &= V_{CC} - R_C I_C \\ &= V_{CC} - \beta \frac{V_{CC} - V_{BE}}{R_B} R_C. \end{aligned}$$

#### Design requirement to avoid saturation region operation

$$V_{CC} - \beta \frac{V_{CC} - V_{BE}}{R_B} R_C > V_{BE}.$$


# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Case – 1 – Simple Biasing

#### □ Challenges

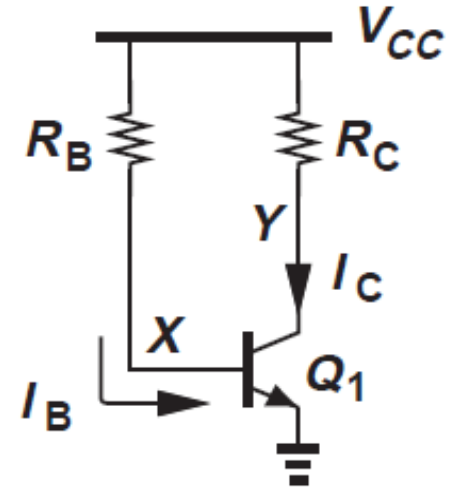- i. The bias is sensitive to  $V_{BE}$  variations
- ii. The bias is sensitive to temperature variations
- iii.  $I_C$  is highly dependent on  $\beta$
- iv. Uncertainty due to  $V_{BE}$  is very pronounced at low  $V_{CC}$ 
  - ✓  $V_{CC} - V_{BE}$  determines the base current
  - ✓ Rarely used for low voltage designs which are very common in modern electronic systems



# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage

#### COMMON EMITTER BIAS CIRCUIT


$$V_{BE} = 0.7 \text{ V (Si)}$$

$$V_{BE} = 0.3 \text{ V (Ge)}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

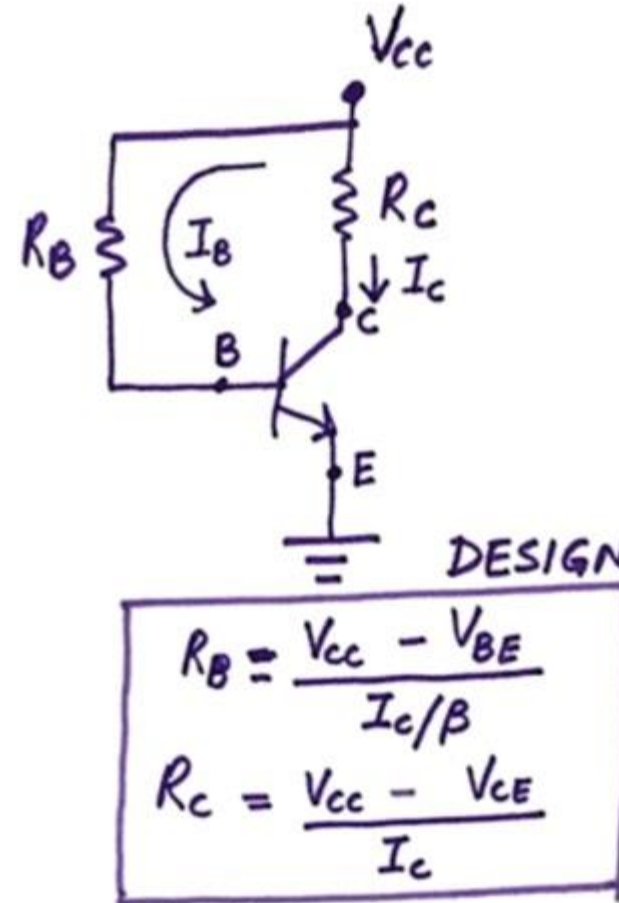


# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### Example 5.7

For the circuit shown in Fig. 5.14, determine the collector bias current. Assume  $\beta = 100$  and  $I_S = 10^{-17}$  A. Verify that  $Q_1$  operates in the forward active region.

Assume  $V_{BE} = 800$  mV

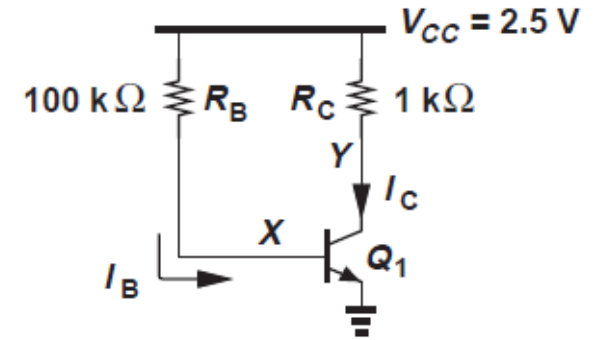




# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage
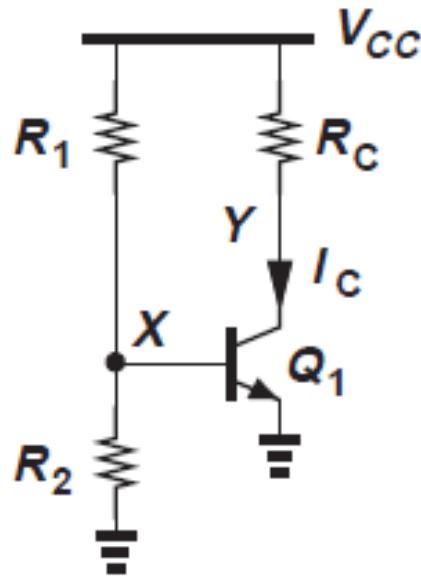
#### □ Case – 2a – Resistor-Divider Biasing without degenerate (Emitter) resistance $R_E$




# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage – Analysis (Simple Method)
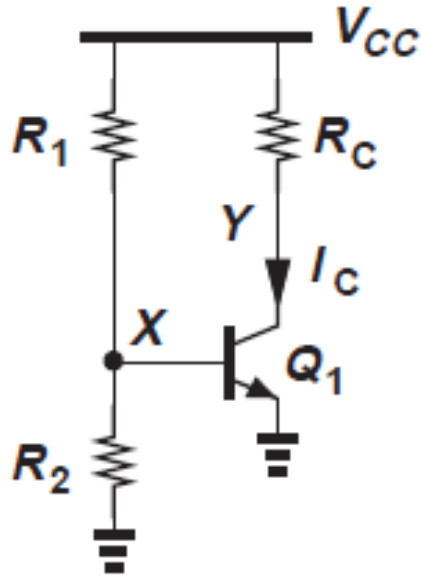
#### □ Case – 2a – Resistor-Divider Biasing without degenerate (Emitter) resistance $R_E$



$$V_X = \frac{R_2}{R_1 + R_2} V_{CC},$$


$$I_C = I_S \exp\left(\frac{R_2}{R_1 + R_2} \cdot \frac{V_{CC}}{V_T}\right),$$

# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage – Analysis (Accurate Method)
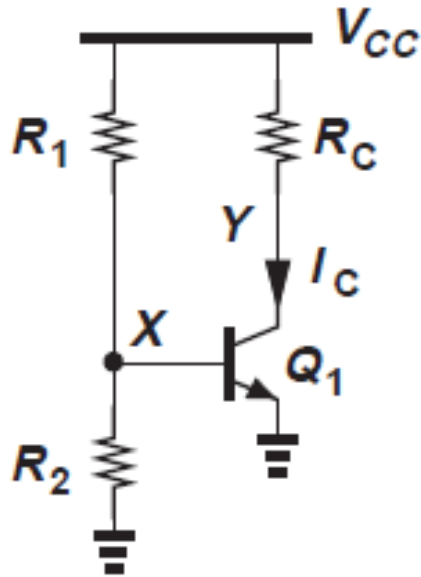
#### □ Case – 2a – Resistor-Divider Biasing without degenerate (Emitter) resistance $R_E$




$$V_{Thev} = \frac{R_2}{R_1 + R_2} V_{CC}.$$

$$R_{Thev} = R_1 || R_2.$$

$$V_X = V_{Thev} - I_B R_{Thev}$$
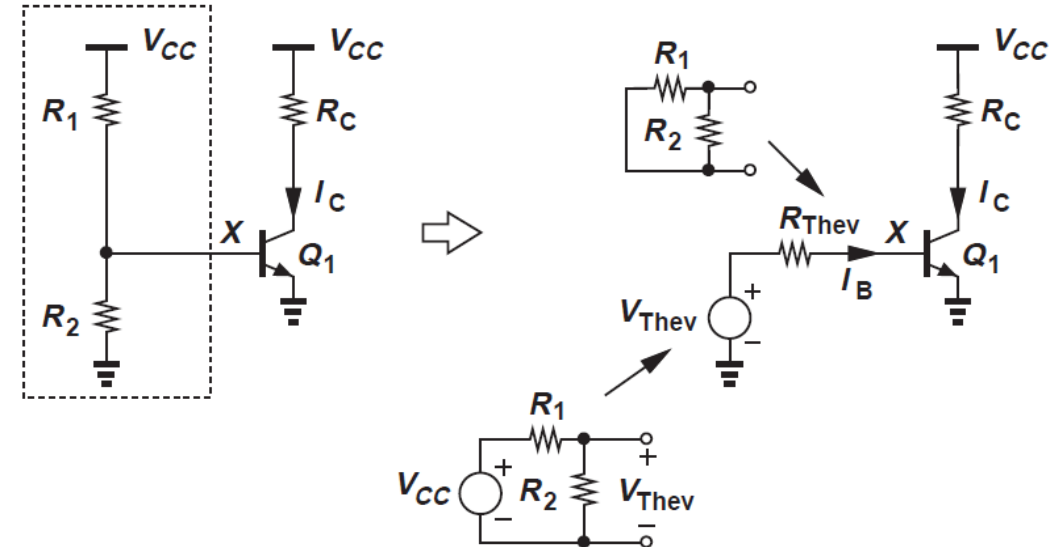
$$I_C = I_S \exp \frac{V_{Thev} - I_B R_{Thev}}{V_T}.$$



# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design


### □ Common Emitter Stage - Analysis

#### □ Case – 2a – Resistor-Divider Biasing without degenerate (Emitter) resistance $R_E$

##### Example 5.9

Calculate the collector current of  $Q_1$  in Fig. 5.18(a). Assume  $\beta = 100$  and  $I_S = 10^{-17}$  A.

Assume  $V_{BE} = 750\text{mV}$

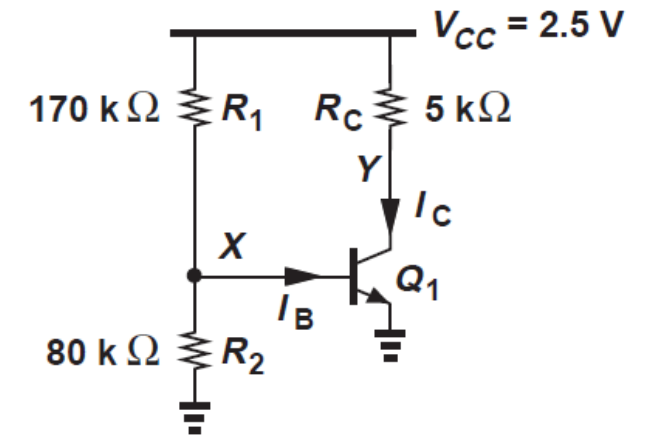

# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage – Advantages and Challenges

#### □ Case – 2a – Resistor-Divider Biasing without degenerate (Emitter) resistance $R_E$


- Proper selection of  $R_1$  and  $R_2$  will make the circuit topology insensitive to  $\beta$
- The  $I_C$  still has exponential dependence to the voltage generated across the  $R_2$  resistance i.e.,  $V_{BE}$
- Variations in the resistance values  $R_1$  and  $R_2$  will result in significant variation in the  $I_C$  values
  - **For example:** 1% variation in the resistor values shall result in ~ 36% variation in the desired  $I_C$  value
- These problems can be adjusted by adding a resistance with the emitter in series i.e.,  $R_E$

# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage
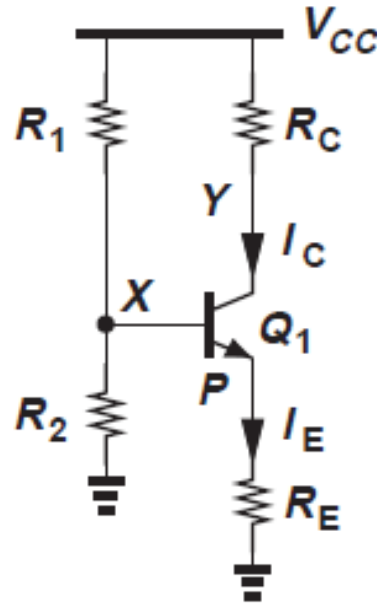
#### □ Case – 2b – Resistor-Divider Biasing with degenerate (Emitter) resistance $R_E$



# Bipolar Amplifiers


## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage – Analysis
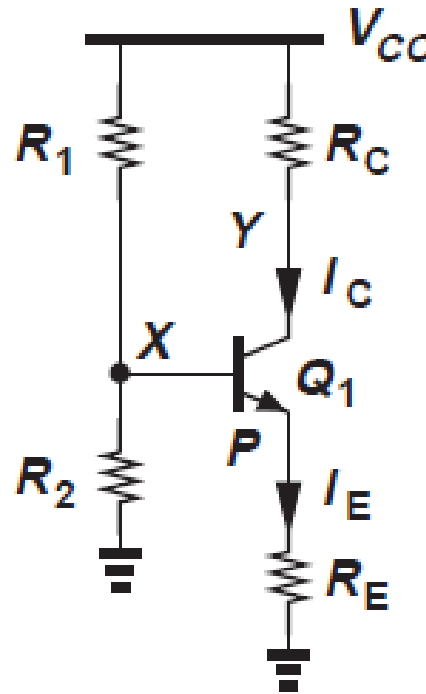
#### □ Case – 2b – Resistor-Divider Biasing with degenerate (Emitter) resistance $R_E$

$$\begin{aligned}V_{CC} &= 12\text{ V} \\ R_1 &= 8.2\text{ k}\Omega \\ R_2 &= 3.9\text{ k}\Omega \\ R_C &= 1\text{ k}\Omega \\ R_E &= 1\text{ k}\Omega\end{aligned}$$

$$\begin{aligned}\beta &= 100 \\ V_{BE} &= 0.7\text{ V} \\ &\text{(Si)}\end{aligned}$$




# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage - Analysis (using Accurate Approach)
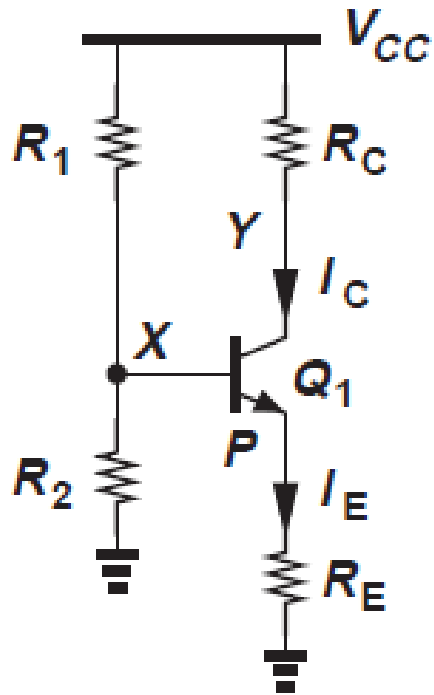
#### □ Case – 2b – Resistor-Divider Biasing with degenerate (Emitter) resistance $R_E$





# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage - Design Approach # 1

#### □ Case – 2b – Resistor-Divider Biasing with degenerate (Emitter) resistance $R_E$


#### DESIGN PROBLEM:

$$\beta = 100, I_{C,Q} = 5\text{mA}$$

$$V_{CE,Q} = 8\text{V}, V_{CC} = 20\text{V}$$

$$V_{BE} = 0.7\text{ (Si)}$$

$$V_E = 20\% \text{ of } V_{CC}$$

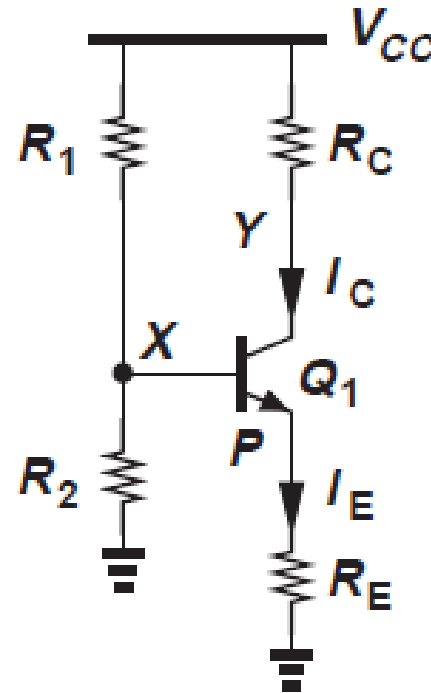

Condition

$$(1 + \beta) R_E \gg R_B$$

# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage - Design Approach # 2

#### □ Case – 2b – Resistor-Divider Biasing with degenerate (Emitter) resistance $R_E$


#### DESIGN PROBLEM:

$$\beta = 100, I_{C,Q} = 5\text{mA}$$

$$V_{CE,Q} = 8\text{V}, V_{CC} = 20\text{V}$$

$$V_{BE} = 0.7\text{ (Si)}$$

$$V_E = 20\% \text{ of } V_{CC}$$

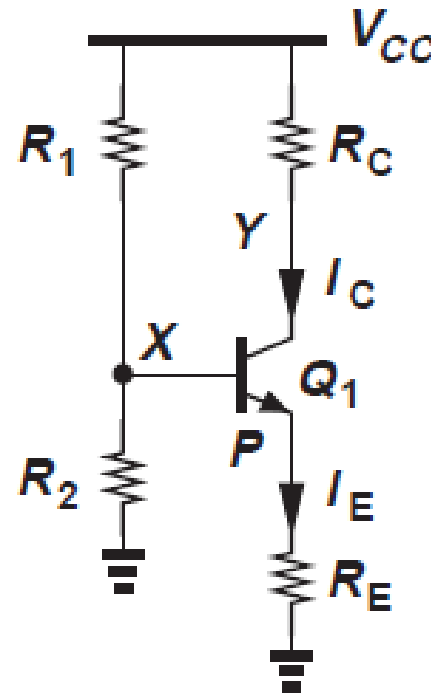

Condition for Design

$$I_1 \gg I_B$$


# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Common Emitter Stage – Advantages and Challenges
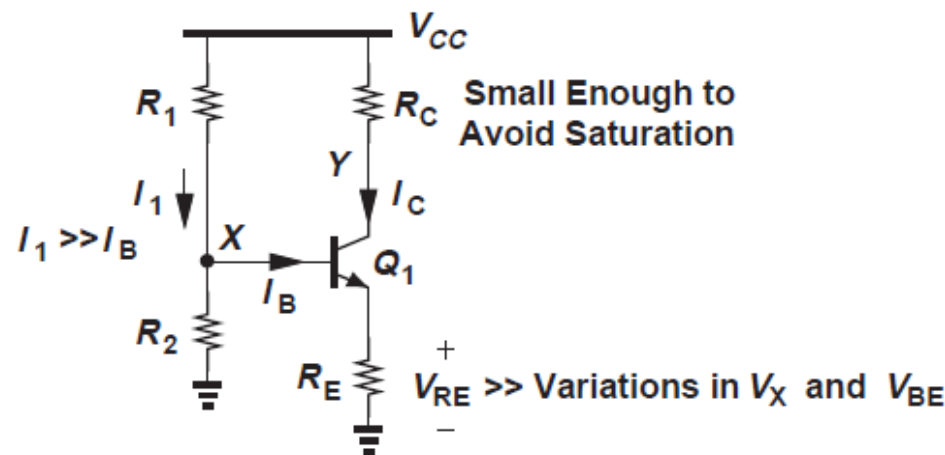
#### □ Case – 2b – Resistor-Divider Biasing with degenerate (Emitter) resistance $R_E$


- This bias topology is extensively used in the discrete circuits and occasionally in the integrated circuits
- The rules for design are
  1.  $I_1 \gg I_B$  to lower the sensitivity of  $\beta$
  2.  $V_{RE}$  must be large enough ( $\sim 100\text{mV}$  or above) to suppress the effect of uncertainties in  $V_X$  and  $V_{BE}$



# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Self-Biased Stage – Analysis

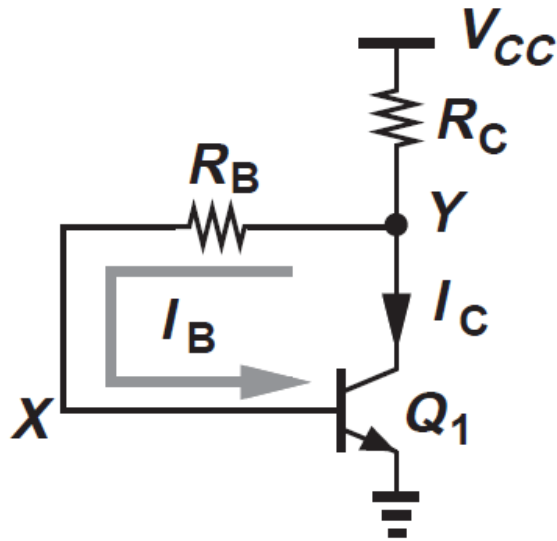

We now determine the collector bias current by assuming  $I_B \ll I_C$ ; i.e.,  $R_C$  carries a current equal to  $I_C$ , thereby yielding

$$V_Y = V_{CC} - R_C I_C. \quad (5.75)$$

Also,

$$V_Y = R_B I_B + V_{BE} \quad (5.76)$$

$$= \frac{R_B I_C}{\beta} + V_{BE}. \quad (5.77)$$

Equating the right-hand sides of Eqs. (5.75) and (5.77) gives

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta}}. \quad (5.78)$$

# Bipolar Amplifiers

## □ Biasing and Operating Point (Q-point) Analysis and Design

### □ Self-Biased Stage – Analysis Example

#### Problem:

Analyze a self-bias circuit with the following values, with and without  $R_E$

$$R_C = R_E = 1 \text{ k}\Omega$$

$$R_B = 150 \text{ k}\Omega$$

$$V_{CC} = 15$$

$$\beta = 150$$


# Bipolar Amplifiers

## □ BJT Amplifier Topologies

□ There are three commonly used topologies for the BJTs

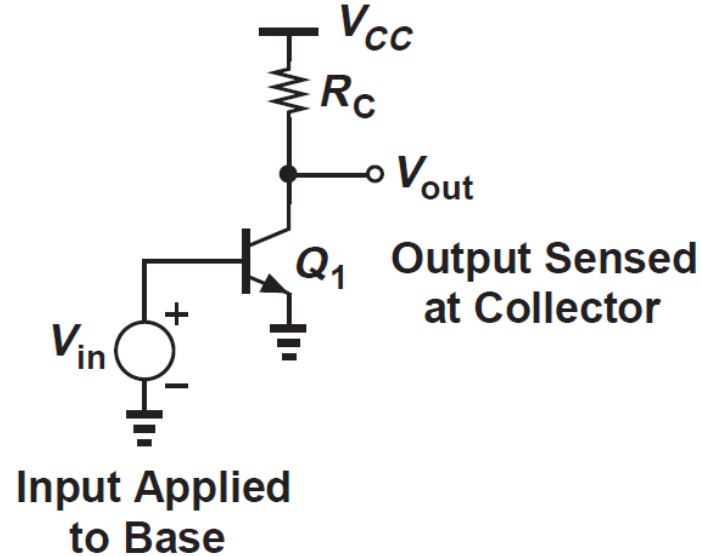1. **Common-Emitter (CE) Topology**
2. Common-Base (CB) Topology
3. Common-Collector Topology

□ In this course we shall only be focusing towards Common-Emitter (CE) Topology





# Bipolar Amplifiers

## □BJT Amplifier Topologies

### □Common-Emitter (CE) Topology

#### □Small Signal Analysis

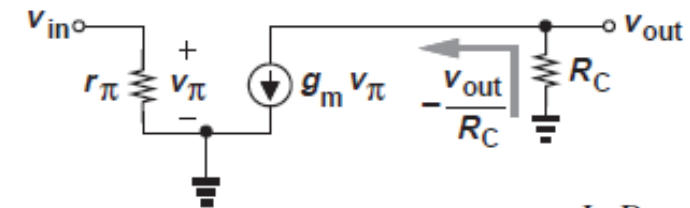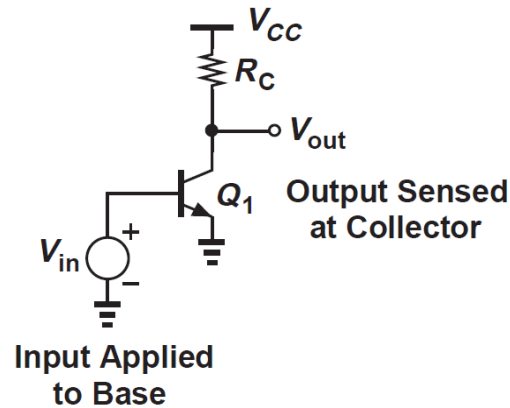

Small-signal model of CE stage.

$$A_v = -g_m R_C.$$

$$|A_v| = \frac{I_C R_C}{V_T}$$
$$= \frac{V_{RC}}{V_T}.$$

Since  $V_{RC} < V_{CC}$ ,

$$|A_v| < \frac{V_{CC}}{V_T}.$$

Furthermore, the transistor itself requires a minimum collector-emitter voltage of about  $V_{BE}$  to remain in the active region, lowering the limit to



$$|A_v| < \frac{V_{CC} - V_{BE}}{V_T}.$$

# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common-Emitter (CE) Topology
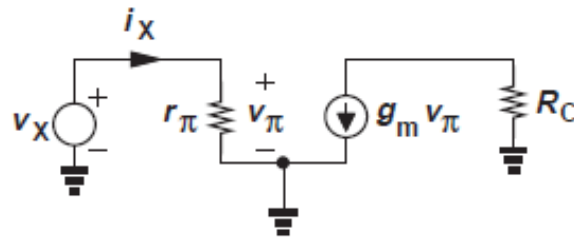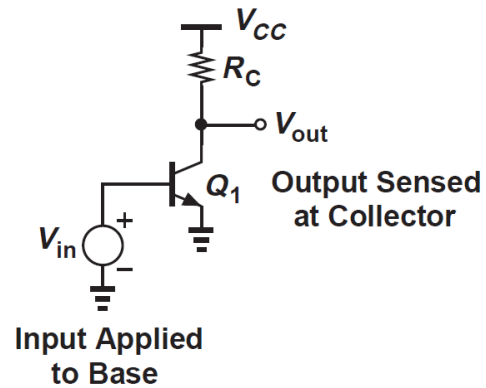
#### □ Small Signal Analysis – Input Impedance Calculation



$$R_{in} = \frac{v_X}{i_X}$$
$$= r_\pi.$$





# Bipolar Amplifiers

## □BJT Amplifier Topologies

### □Common-Emitter (CE) Topology
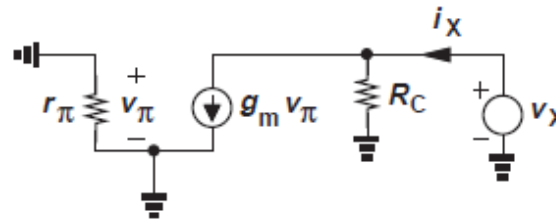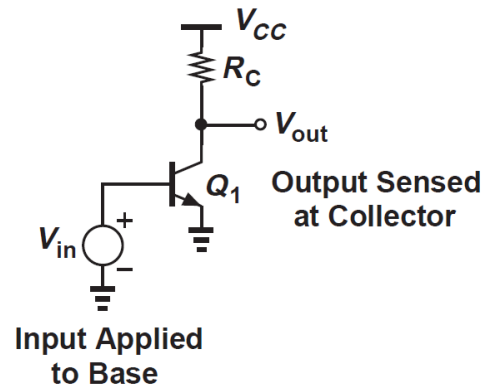
#### □Small Signal Analysis – Output Impedance Calculation





$$R_{out} = \frac{v_X}{i_X}$$
$$= R_C.$$

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### □Common-Emitter (CE) Topology – CE Stage Trade Offs

Figure 5.33 summarizes the trade-offs in the performance of the CE topology along with the parameters that create such trade-offs. For example, for a given value of output impedance,  $R_C$  is fixed and the voltage gain can be increased by increasing  $I_C$ , thereby lowering both the voltage headroom and the input impedance.

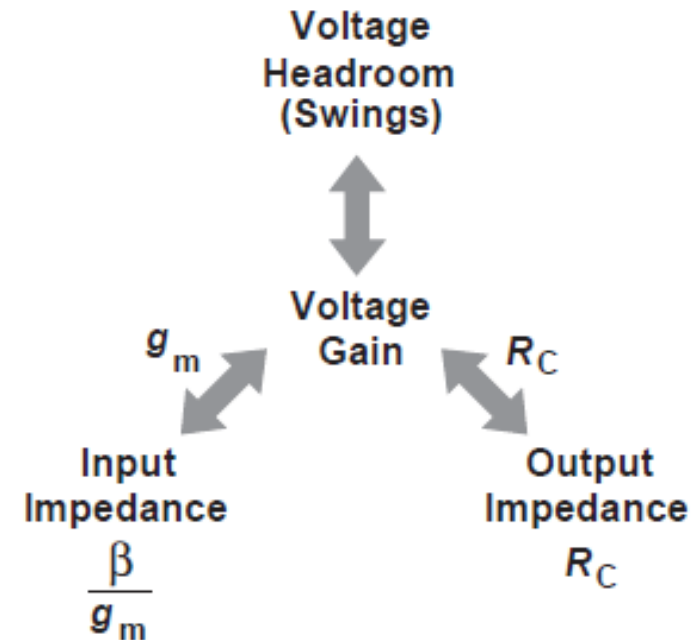
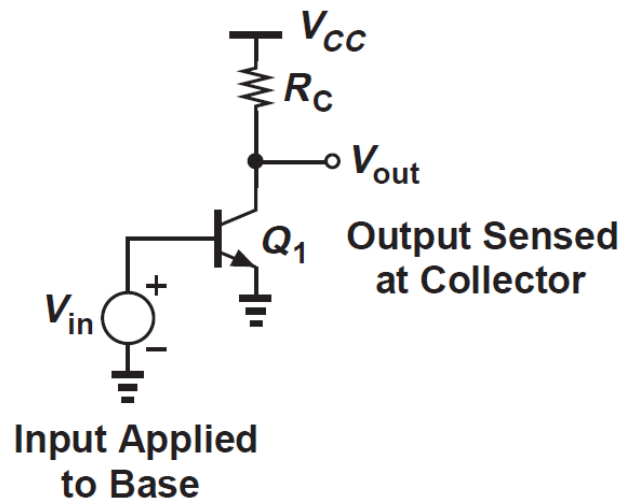


# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology

#### □ With Early Effect

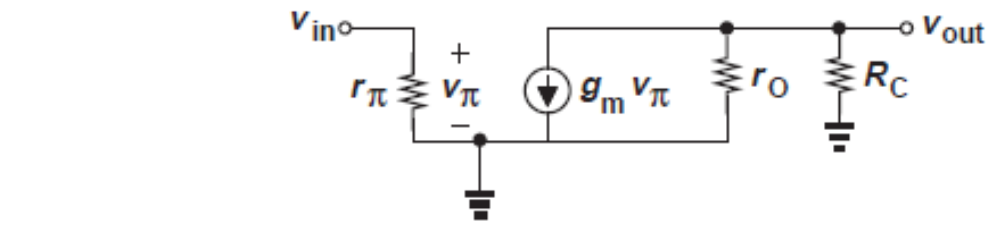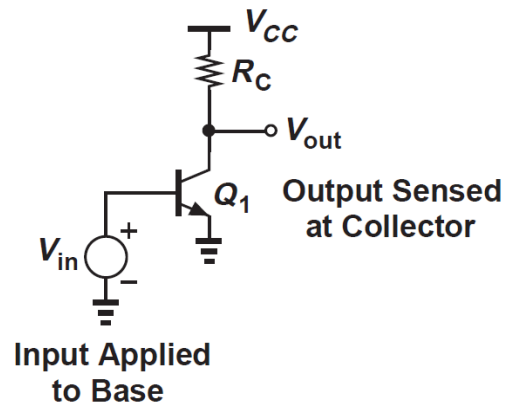

CE stage including Early effect.

$$R_{in} = r_\pi$$

$$R_{out} = R_C || r_o.$$

$$A_v = -g_m(R_C || r_o).$$

$$A_I = \frac{i_{out}}{i_{in}},$$



# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology

#### □ With Emitter Degenerate Resistance $R_E$ (without Early Effect)

##### □ Small-Signal Model

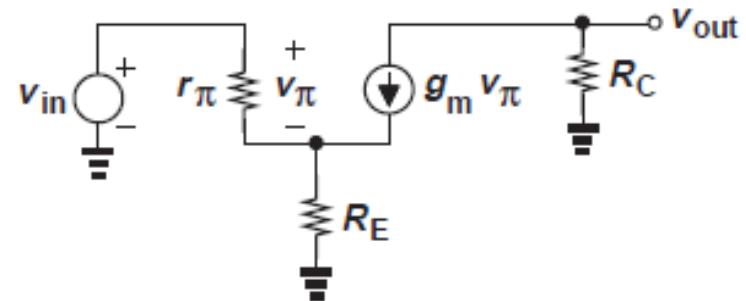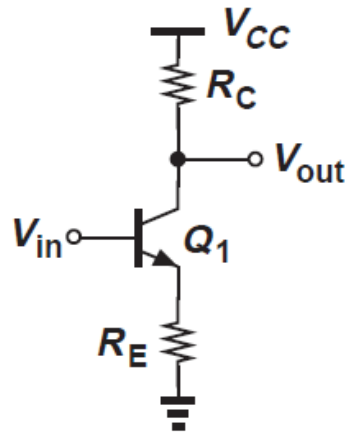


# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology

#### □ With Emitter Degenerate Resistance $R_E$ (without Early Effect)

##### □ Voltage Gain Calculation

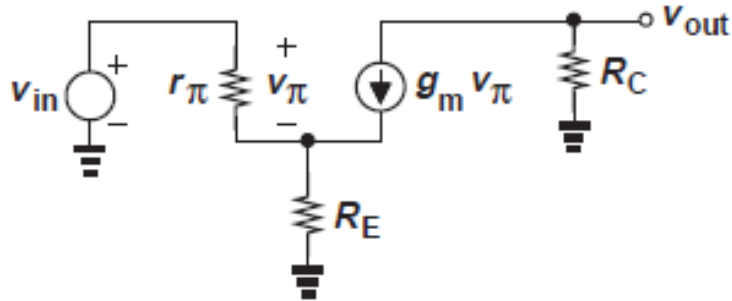

@ Output Node (Apply KCL)

$$g_m v_{\pi} = -\frac{v_{out}}{R_C},$$

$$v_{\pi} = -\frac{v_{out}}{g_m R_C}.$$

Voltage drop across  $R_E$

$$v_{RE} = \left( \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} \right) R_E.$$

$$v_{in} = v_{\pi} + v_{RE}$$

$$= v_{\pi} + \left( \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} \right) R_E$$

$$= v_{\pi} \left[ 1 + \left( \frac{1}{r_{\pi}} + g_m \right) R_E \right].$$

$$\frac{v_{out}}{v_{in}} = -\frac{g_m R_C}{1 + \left( \frac{1}{r_{\pi}} + g_m \right) R_E}.$$

For  $\beta \gg 1$ , results in  $g_m \gg 1 / r_{\pi}$

$$A_v = -\frac{g_m R_C}{1 + g_m R_E}.$$


# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology

□ With Emitter Degenerate Resistance  $R_E$  (without Early Effect)

□ Input Resistance Calculation

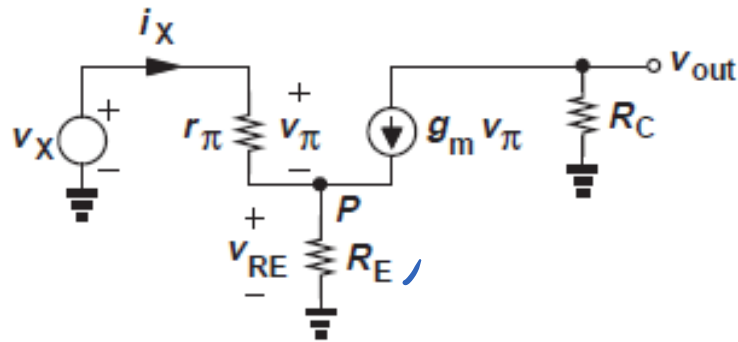

$$v_X = r_\pi i_X + R_E(1 + \beta)i_X,$$

$$R_{in} = \frac{v_X}{i_X}$$

$$= r_\pi + (\beta + 1)R_E.$$


# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology

#### □ With Emitter Degenerate Resistance $R_E$ (without Early Effect)

##### □ Output Resistance Calculation

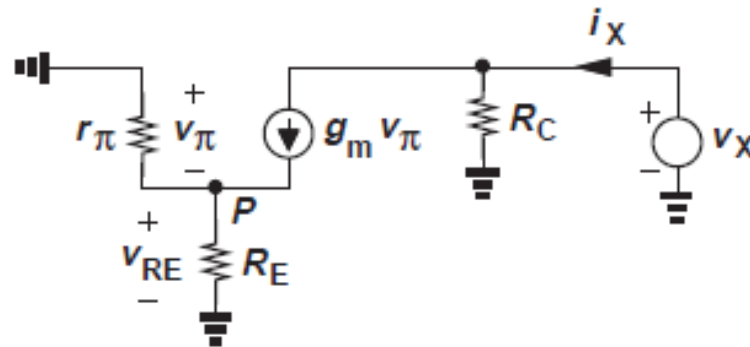

$$v_{in} = 0 = v_\pi + \left( \frac{v_\pi}{r_\pi} + g_m v_\pi \right) R_E,$$

yielding  $v_\pi = 0$  and hence  $g_m v_\pi = 0$ . Thus, all of  $i_X$  flows through  $R_C$ , and

$$\begin{aligned} R_{out} &= \frac{v_X}{i_X} \\ &= R_C, \end{aligned}$$

# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology

#### □ With Emitter Degenerate Resistance $R_E$ (without Early Effect)

##### □ Advantages of Emitter Degenerate Resistance ( $R_E$ )

- ✓ If  $g_m R_E \gg 1$ , the voltage gain becomes independent of transconductance ( $g_m$ ) and in effect, the biasing current  $I_C$

$$A_v \rightarrow -R_C / R_E$$



# Bipolar Amplifiers

## □ BJT Amplifier Topologies


### □ Common Emitter Topology

□ With Emitter Degenerate Resistance  $R_E$  (without Early Effect) and Base Resistance ( $R_B$ )

#### □ Analysis

To analyze the small-signal behavior of this stage, we can adopt one of two approaches:

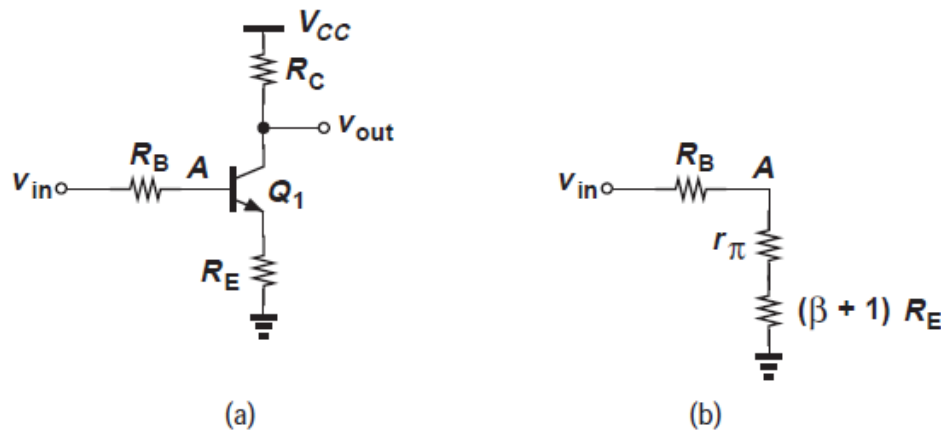- (a) draw the small-signal model of the entire circuit and solve the resulting equations, or
- (b) recognize that the signal at node  $A$  is simply an attenuated version of  $v_{in}$  and write



$$\frac{v_{out}}{v_{in}} = \frac{v_A}{v_{in}} \cdot \frac{v_{out}}{v_A}.$$

$$\frac{v_A}{v_{in}} = \frac{r_{\pi} + (\beta + 1)R_E}{r_{\pi} + (\beta + 1)R_E + R_B}.$$

(a) CE stage with base resistance, (b) equivalent circuit.


# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology

□ With Emitter Degenerate Resistance  $R_E$  (without Early Effect) and Base Resistance ( $R_B$ )

□ Analysis

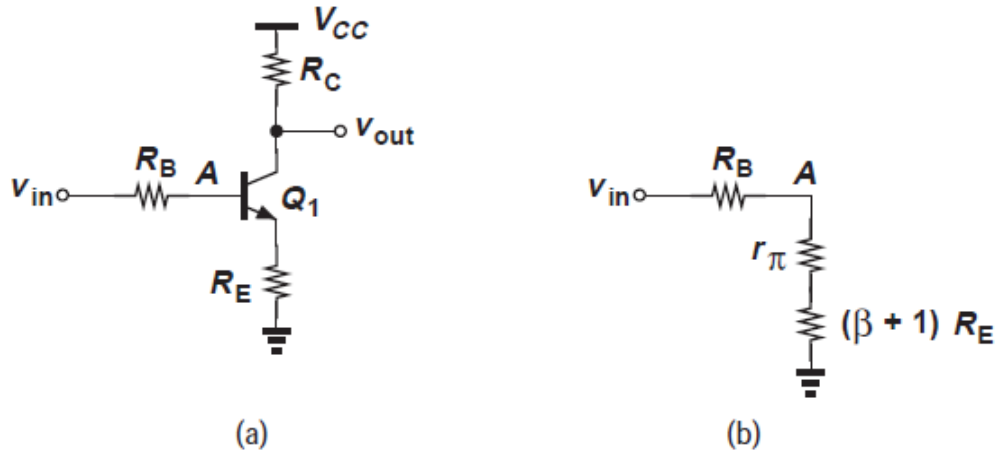

(a) CE stage with base resistance, (b) equivalent circuit.

$$\frac{v_{out}}{v_{in}} = \frac{v_A}{v_{in}} \cdot \frac{v_{out}}{v_A}$$

$$\frac{v_A}{v_{in}} = \frac{r_{\pi} + (\beta + 1)R_E}{r_{\pi} + (\beta + 1)R_E + R_B}$$

$$\begin{aligned} \frac{v_{out}}{v_{in}} &= \frac{r_{\pi} + (\beta + 1)R_E}{r_{\pi} + (\beta + 1)R_E + R_B} \cdot \frac{-g_m R_C}{1 + \left(\frac{1}{r_{\pi}} + g_m\right)R_E} \\ &= \frac{r_{\pi} + (\beta + 1)R_E}{r_{\pi} + (\beta + 1)R_E + R_B} \cdot \frac{-g_m r_{\pi} R_C}{r_{\pi} + (1 + \beta)R_E} \\ &= \frac{-\beta R_C}{r_{\pi} + (\beta + 1)R_E + R_B} \end{aligned}$$

$$A_v \approx \frac{-R_C}{\frac{1}{g_m} + R_E + \frac{R_B}{\beta + 1}}$$


# Bipolar Amplifiers

## □ BJT Amplifier Topologies


### □ Common Emitter Topology

□ With Emitter Degenerate Resistance  $R_E$  (without Early Effect) and Base Resistance ( $R_B$ )

□ Analysis

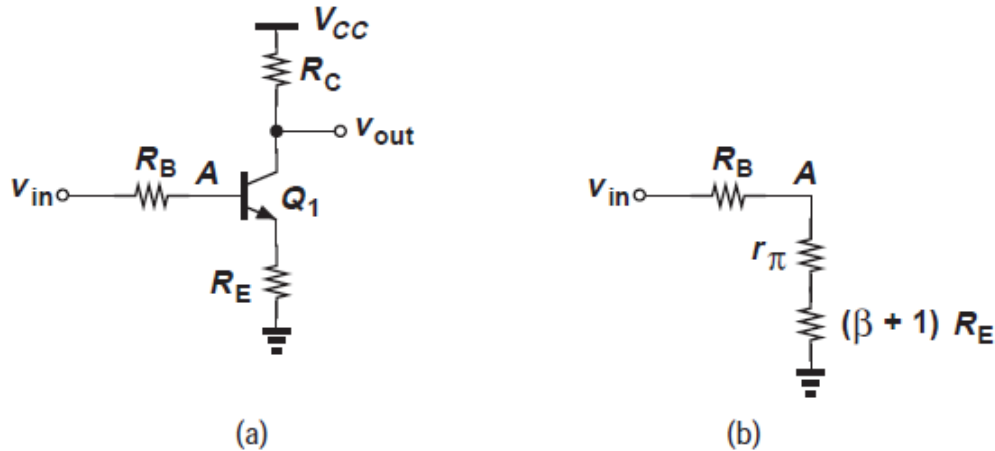

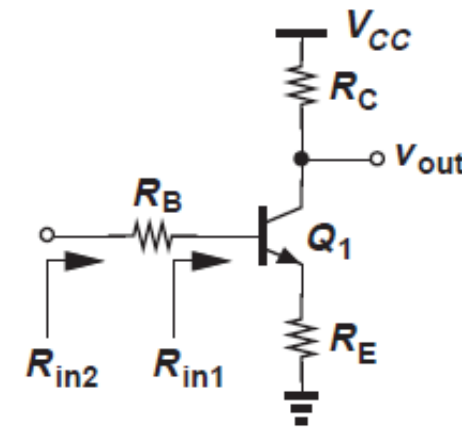(a) CE stage with base resistance, (b) equivalent circuit.



$$R_{in1} = r_\pi + (\beta + 1)R_E$$

$$R_{in2} = R_B + r_\pi + (\beta + 1)R_E.$$

$$R_{out} = R_C$$

# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology


#### □ With Emitter Degenerate Resistance $R_E$ (without Early Effect) and Base Resistance ( $R_B$ )

##### □ Challenges of Base Resistance ( $R_B$ )


- ✓ Base resistance degrades the performance

Gain without  $R_B$

$$A_v = -\frac{g_m R_C}{1 + g_m R_E}$$

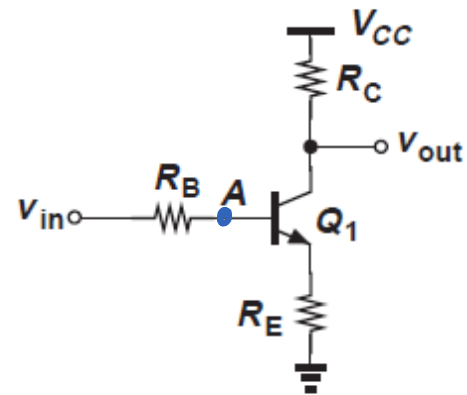

(a)

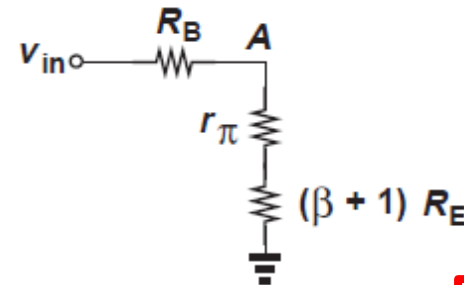

(b)

(a) CE stage with base resistance, (b) equivalent circuit.

Gain with  $R_B$

$$A_v \approx \frac{-R_C}{\frac{1}{g_m} + R_E + \frac{R_B}{\beta + 1}}$$


# Bipolar Amplifiers

## □ BJT Amplifier Topologies


### □ Common Emitter Topology
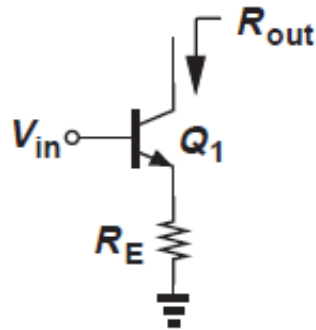
#### □ With Emitter Degenerate Resistance $R_E$ with Early Effect

- Early Effect primarily affects the output impedance of the circuit
- Let us calculate the output impedance with the early effect



(a)

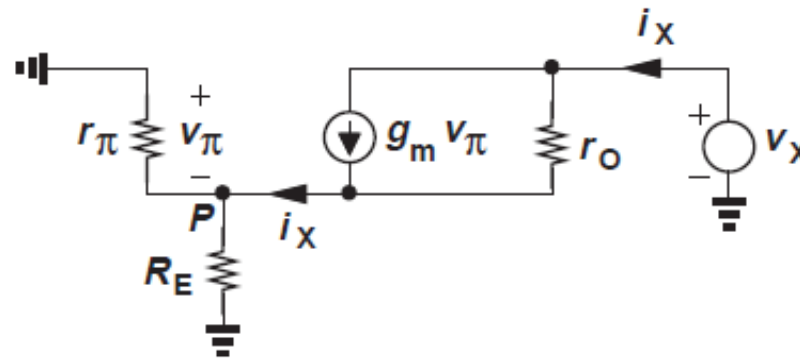

(b)


(a) Output impedance of degenerated stage, (b) equivalent circuit.

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### □Common Emitter Topology
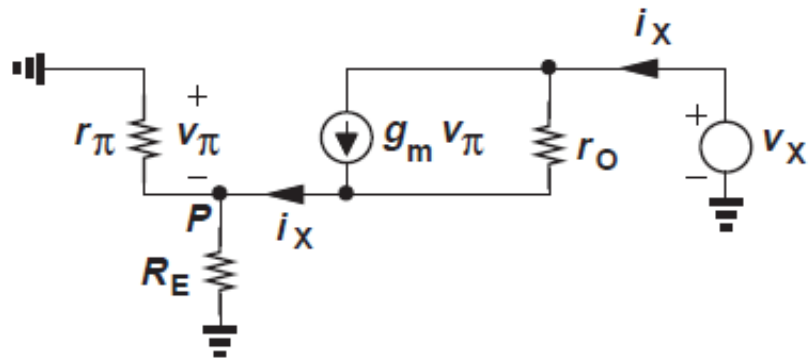
#### □With Emitter Degenerate Resistance $R_E$ with Early Effect



$$v_\pi = -i_X(R_E || r_\pi),$$

$$\begin{aligned} v_X &= (i_X - g_m v_\pi)r_O - v_\pi \\ &= [i_X + g_m i_X(R_E || r_\pi)]r_O + i_X(R_E || r_\pi). \end{aligned}$$

The output resistance is boosted by  $(1 + g_m R_E)$  with the inclusion of Early Effect

$$\begin{aligned} R_{out} &= [1 + g_m(R_E || r_\pi)]r_O + R_E || r_\pi \\ &= r_O + (g_m r_O + 1)(R_E || r_\pi). \end{aligned}$$

the intrinsic gain of the transistor,  $g_m r_O \gg 1$ .

$$\begin{aligned} R_{out} &\approx r_O + g_m r_O(R_E || r_\pi) \\ &\approx r_O[1 + g_m(R_E || r_\pi)]. \end{aligned}$$

For  $R_E \gg r_\pi$ , we have  $R_E || r_\pi \rightarrow r_\pi$  and

$$\begin{aligned} R_{out} &\approx r_O(1 + g_m r_\pi) \\ &\approx \beta r_O, \end{aligned}$$

For  $R_E \ll r_\pi$ , we have  $R_E || r_\pi \rightarrow R_E$  and

$$R_{out} \approx (1 + g_m R_E)r_O.$$

# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter Topology

#### □ Common Emitter with Biasing



- Remember that we have seen three biasing schemes
  - Simple (Base Resistance) Biasing
  - Resistor-Divider Biasing
  - Self Biasing

# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter with Biasing

#### □ Case – 1 – Simple Biasing

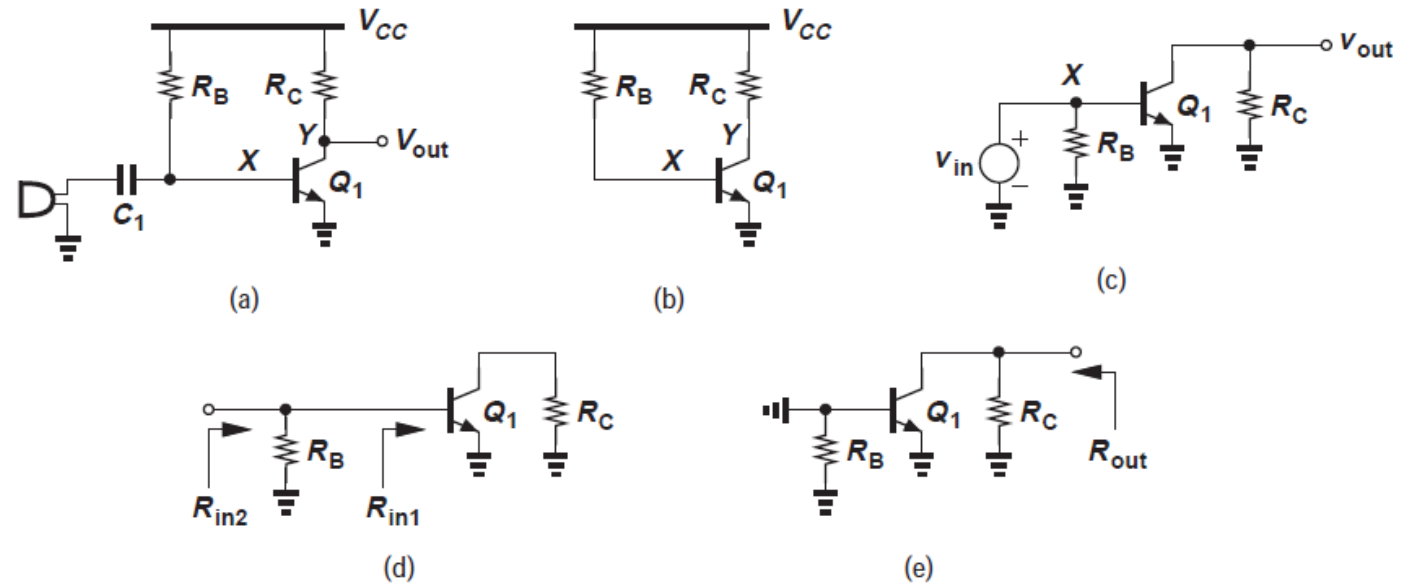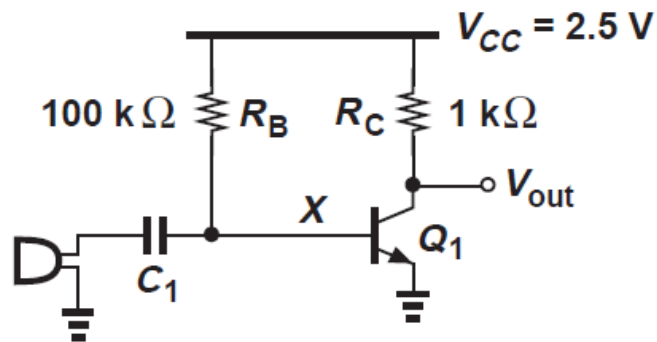

**Figure 5.52** (a) Capacitive coupling at the input of a CE stage, (b) simplified stage for bias calculation, (c) simplified stage for small-signal calculation, (d) simplified circuit for input impedance calculation, (e) simplified circuit for output impedance calculation.




# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter with Biasing

#### □ Case – 1 – Simple Biasing

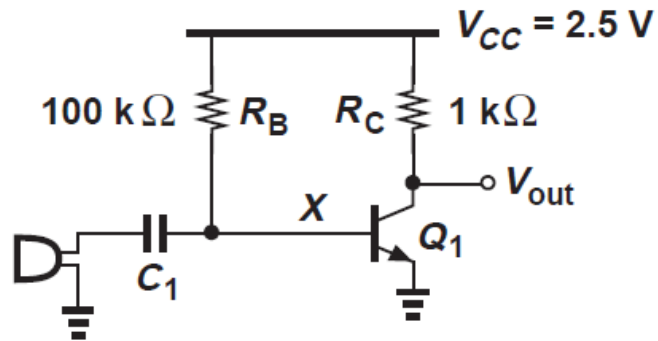

#### DC Analysis

$$I_C = \beta \frac{V_{CC} - V_{BE}}{R_B},$$

$$V_Y = V_{CC} - \beta R_C \frac{V_{CC} - V_{BE}}{R_B}.$$

To avoid saturation,  $V_Y \geq V_{BE}$ .

#### Voltage Gain

$$\frac{v_{out}}{v_{in}} = -g_m(R_C || r_o).$$

#### Input Impedance

$$R_{in2} = r_\pi || R_B.$$

#### Output Impedance


$$R_{out} = R_C || r_o.$$

# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### □ Common Emitter with Biasing
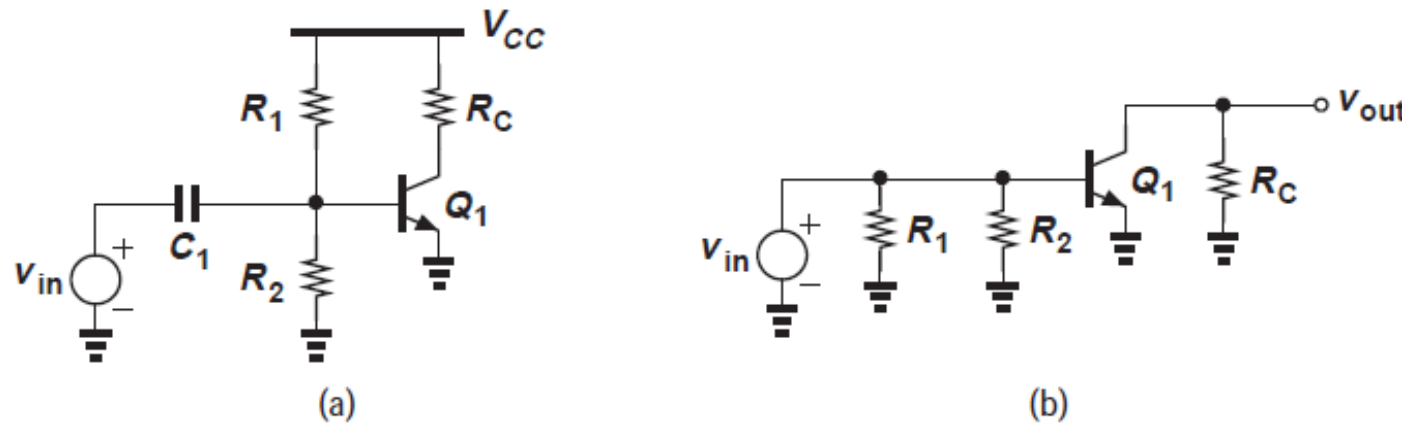
#### □ Case – 2a – Voltage Divider Biasing (with Early Effect)



(a) Biased stage with capacitive coupling, (b) simplified circuit.

Voltage Gain

$$-g_m(R_C || r_o)$$

Input Impedance

$$R_{in} = r_{\pi} || R_1 || R_2.$$

Output Impedance



$$R_{out} = R_C$$

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### □Common Emitter with Biasing
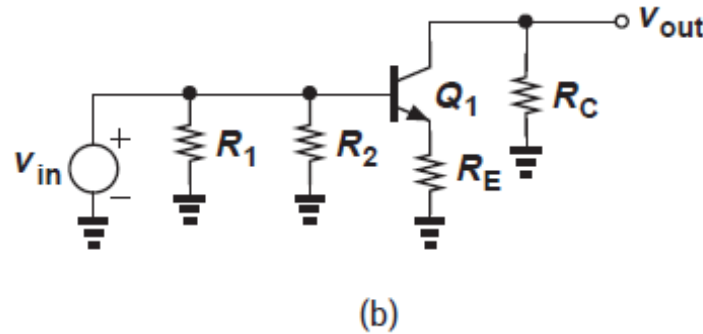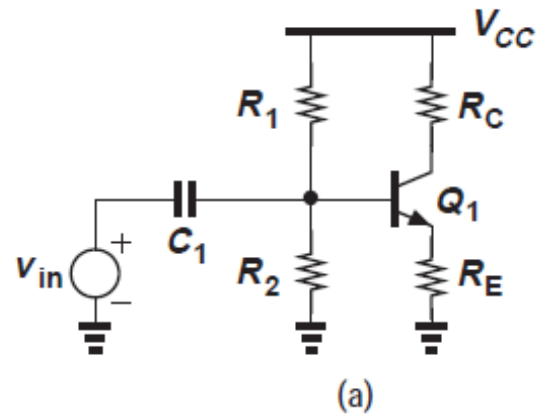
#### □Case – 2b – Voltage Divider Biasing with Emitter Degenerate Resistance



(a) Degenerated stage with capacitive coupling, (b) simplified circuit.

#### Voltage Gain

$$A_v = \frac{-R_C}{\frac{1}{g_m} + R_E},$$

#### Input Impedance

$$R_{in} = [r_\pi + (\beta + 1)R_E] || R_1 || R_2,$$

#### Output Impedance


$$R_{out} = R_C$$

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### □Common Emitter with Biasing
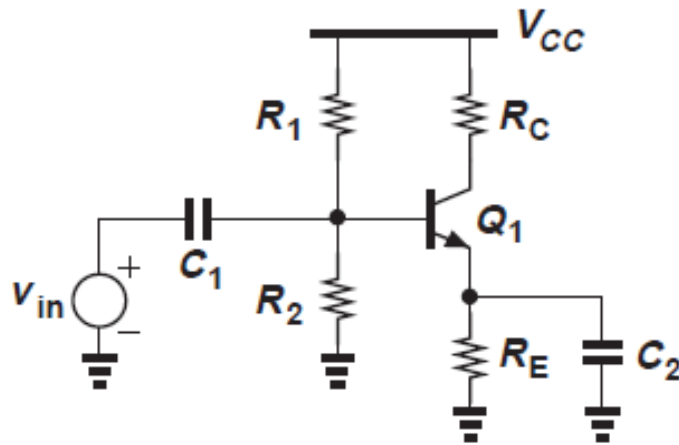
#### □Use of Capacitor to Eliminate Degenerate



#### Advantages

- The use of  $R_E$  provides biasing linearity and stability but decreases the gain
- Using capacitor eliminates  $R_E$  effect on the small-signal gain

#### Voltage Gain

$$A_v = -g_m R_C$$

#### Input Impedance

$$R_{in} = r_{\pi} || R_1 || R_2$$

#### Output Impedance

$$R_{out} = R_C.$$

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### □Common Emitter with Biasing

#### □A general (practical) CE stage (without Early Effect)

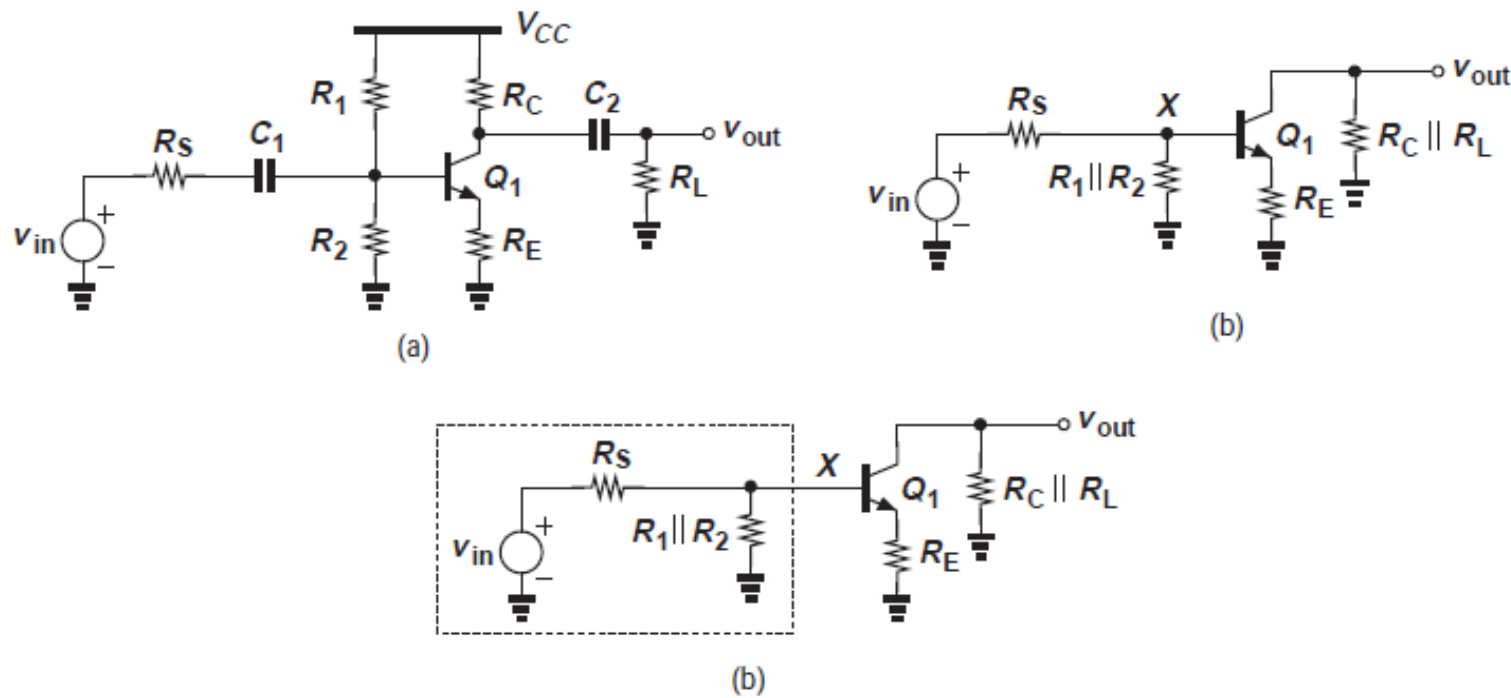


Figure 5.58 (a) General CE stage, (b) simplified circuit, (c) Thevenin model of input network.

#### Voltage Gain

$$A_v = - \frac{R_C \parallel R_L}{\frac{1}{g_m} + R_E + \frac{R_{Thev}}{\beta + 1}} \cdot \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S},$$

#### Input Impedance (between $R_S$ and node X)

$$R_1 \parallel R_2 \parallel [r_\pi + (\beta + 1)R_E]$$

#### Output Impedance

$$R_C \parallel R_L$$

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### Example 5.20


A CE stage must achieve an input impedance of  $R_{in}$  and an output impedance of  $R_{out}$ .  
What is the voltage gain of the circuit?

# Bipolar Amplifiers

## □BJT Amplifier Topologies
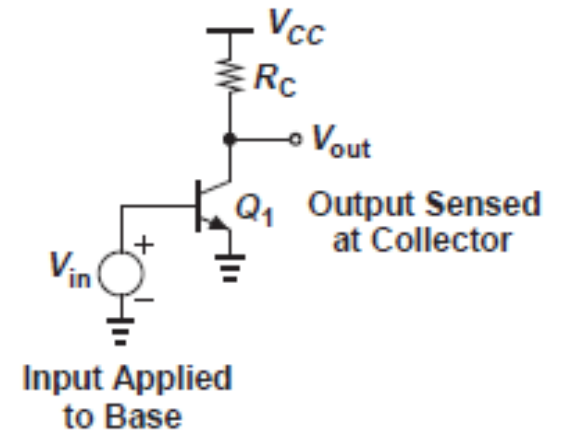
### Example 5.21

The circuit of Fig. 5.29 is biased with a collector current of 1 mA and  $R_C = 1\text{ k}\Omega$ . If  $\beta = 100$  and  $V_A = 10\text{ V}$ , determine the small-signal voltage gain and the I/O impedances.



# Bipolar Amplifiers

## □BJT Amplifier Topologies

### Example 5.22

Determine the voltage gain of the stage shown in Fig. 5.37(a).

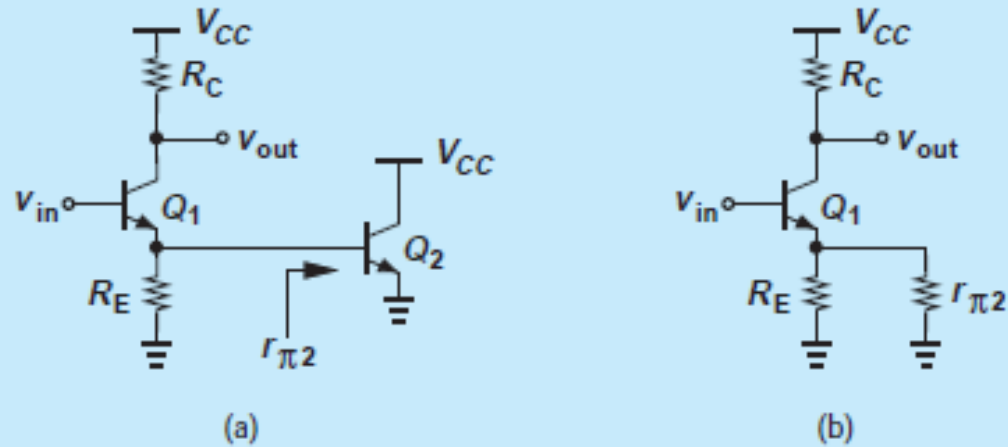


Figure 5.37 (a) CE stage example, (b) simplified circuit.



# Bipolar Amplifiers

## □ BJT Amplifier Topologies

### Example 5.23

Calculate the voltage gain of the circuit in Fig. 5.38(a).

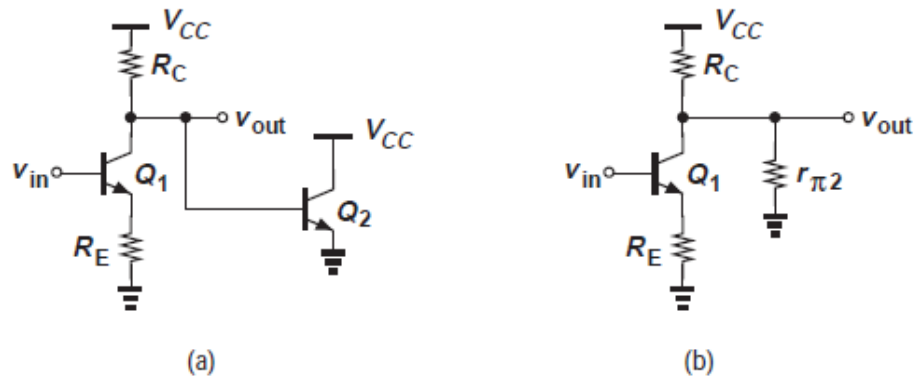


Figure 5.38 (a) CE stage example, (b) simplified circuit.

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### Example 5.24

A CE stage is biased at a collector current of 1 mA. If the circuit provides a voltage gain of 20 with no emitter degeneration and 10 with degeneration, determine  $R_C$ ,  $R_E$ , and the I/O impedances. Assume  $\beta = 100$ .

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### Example 5.27

Determine the voltage gain and I/O impedances of the circuit shown in Fig. 5.45(a). Assume a very large value for  $C_1$  and neglect the Early effect.

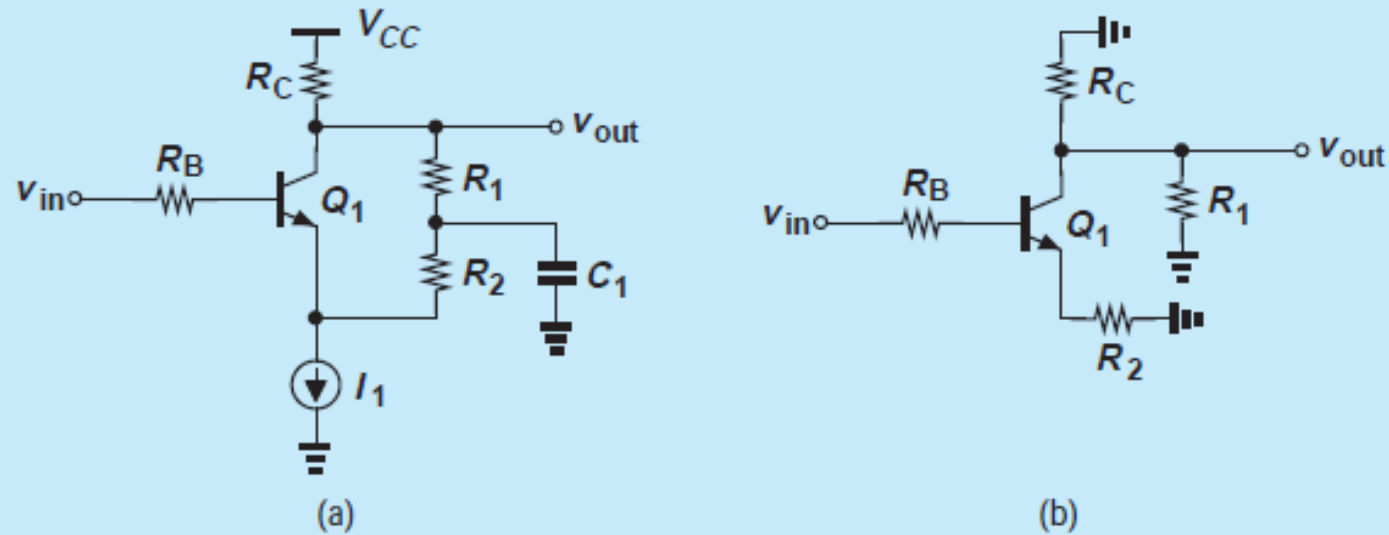


Figure 5.45 (a) CE stage example, (b) simplified circuit.

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### Example 5.28

We wish to design a current source having a value of 1 mA and an output resistance of 20 k $\Omega$ . The available bipolar transistor exhibits  $\beta = 100$  and  $V_A = 10$  V. Determine the minimum required value of emitter degeneration resistance.

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### Example 5.29

Calculate the output resistance of the circuit shown in Fig. 5.48(a) if  $C_1$  is very large.

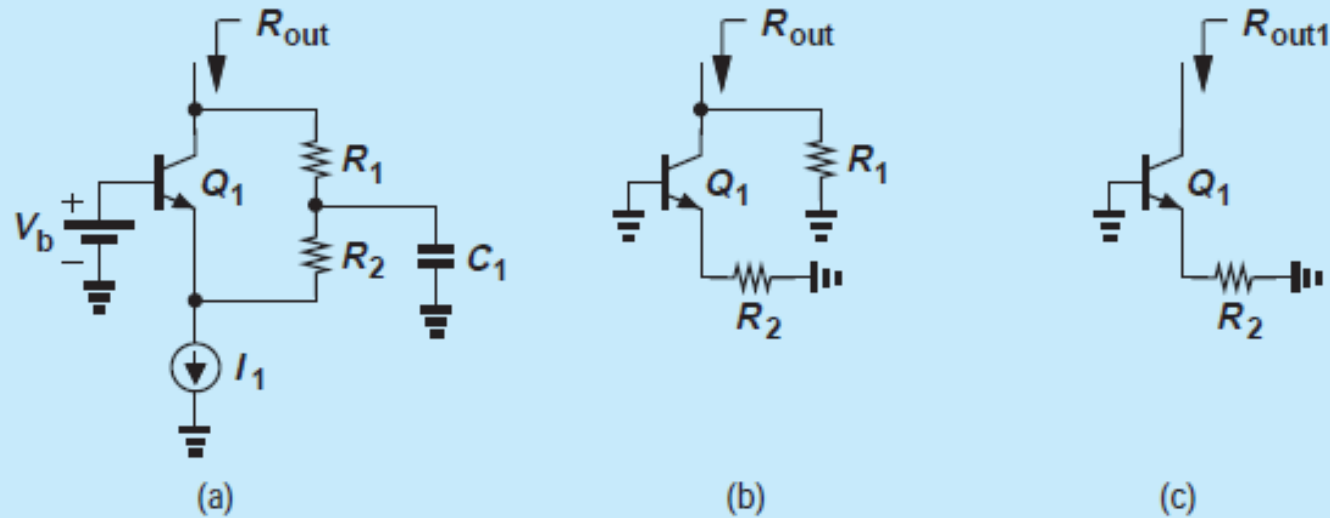


Figure 5.48 (a) CE stage example, (b) simplified circuit, (c) resistance seen at the collector.

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### Example 5.30

Determine the output resistance of the stage shown in Fig. 5.49(a).

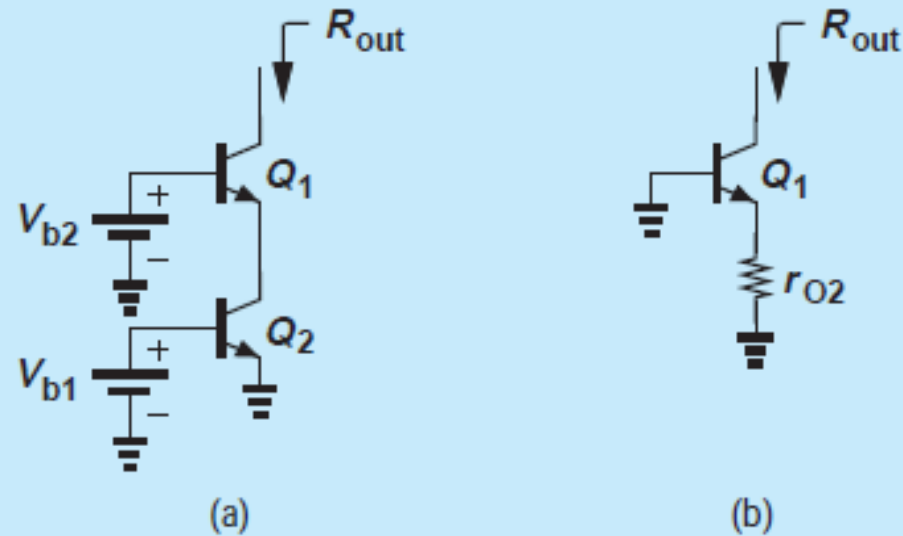


Figure 5.49 (a) CE stage example, (b) simplified circuit.

# Bipolar Amplifiers

## □BJT Amplifier Topologies

### Example 5.34

Design the stage of Fig. 5.57 to satisfy the following conditions:  $I_C = 1$  mA, voltage drop across  $R_E = 400$  mV, voltage gain = 20 in the audio frequency range (20 Hz to 20 kHz), input impedance  $> 2$  k $\Omega$ . Assume  $\beta = 100$ ,  $I_S = 5 \times 10^{-16}$ , and  $V_{CC} = 2.5$  V.