



Habib University

Electrical Engineering Department

Dhanani School of Science & Engineering

Course	EE – 211 – Basic Electronics
Semester	Fall 2022
Section	Section L2
Exam	Quiz – 3a
Instructor	Dr. Ahmad Usman
Total Marks	10

Question – 1 (Points: 1.5 + 5 + 1.5 + 2)

Consider an npn transistor-based amplifier circuit, biased in common emitter configuration, and having the following parameters: $V_{CC} = 2.5\text{ V}$, $I_S = 3 \times 10^{-16}\text{ A}$, $R_C = 100\text{ }\Omega$, $V_{BE} = 800\text{ mV}$, $\beta = 100$. The amplifier is having a microphone attached at the input (i.e., base terminal) and the amplified output is observed at the collector terminal.

- Draw the circuit diagram of the amplifier circuit clearly representing each of the important components.
- Calculate I_C , I_B , I_E , V_{CE} , g_m , and r_{π} .
- Draw the equivalent small-signal model of the transistor. Assume no-early effect.
- Assuming a 2 mV of input signal at the microphone, calculate the amplified signal voltage at the output.

*Bonus: (Points: 3)

Does the input signal qualifies as a small-signal? Calculate the voltage swing at the output with respect to the Q-point of the circuit. Does the transistor remain in forward active region of operation or not? Use your calculations to justify your answer.

Assuming $V_T \approx 26\text{ mV}$


$$(b) \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$I_C = 6.918\text{ mA}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_B = 69.187\text{ }\mu\text{A}$$

$$I_E = I_C + I_B = 6.9871\text{ mA}$$

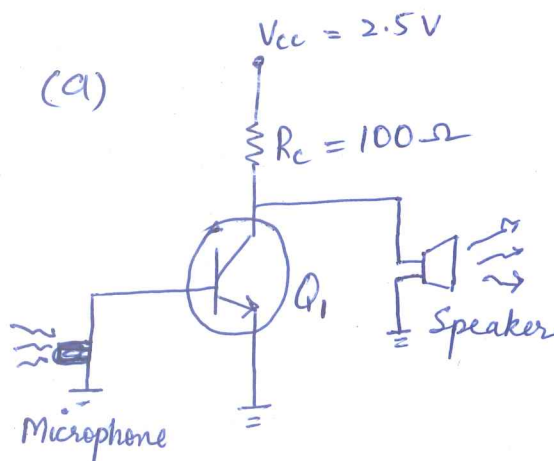

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = 1.8082\text{ V}$$


$$g_m = \frac{I_C}{V_T}$$

$$g_m = 0.26607\text{ }\Omega^{-1}$$

$$r_{\pi} = \beta / g_m$$

$$r_{\pi} = 375.831\text{ }\Omega$$

(C) Small Signal Model

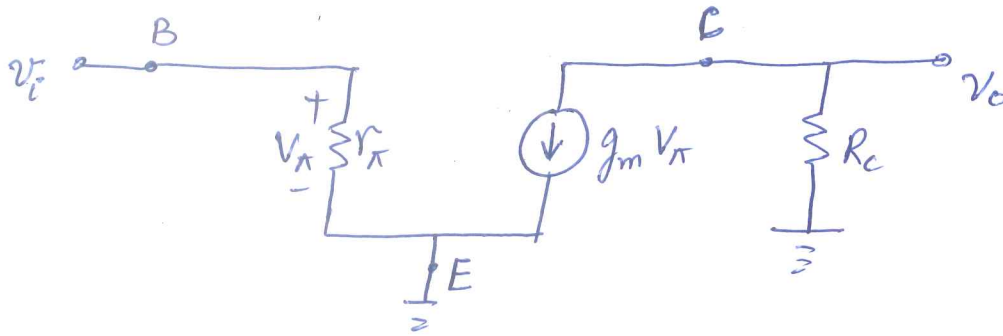

(d)

$$\Delta i_c = g_m \Delta V_{BE}$$

$$\Delta V_{BE} = v_{in} = 2 \text{ mV}$$



$$\Delta i_c = 0.266 \times 2 \text{ m} = \underline{0.532 \text{ mA}}$$

$$\Delta V_{out} = (\Delta i_c) R_c = \underline{53.2 \text{ mV}}$$

The voltage amplified by a factor of 26.6.

BONUS

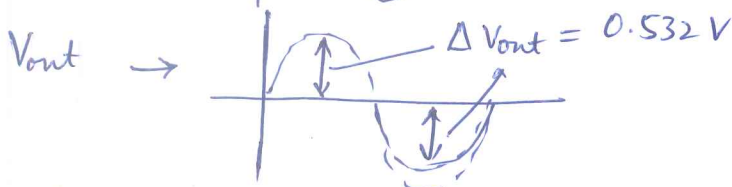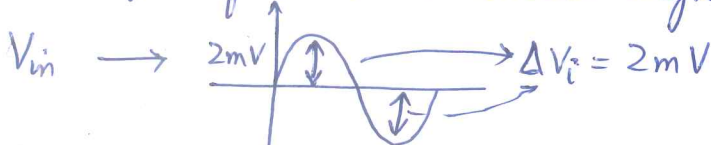The input signal is less than 1% of the V_{CC} .
It qualifies as a small-signal.



$$\underline{V_{CE,Q} = 1.8082 \text{ V}}$$

$$V_{CE(\text{max})} = 2.3402 \text{ V}$$

$$V_{CE(\text{min})} = 1.2762 \text{ V}$$

For $V_{CE(\text{max})}$


$$V_{BE} = 0.8 \text{ V} \quad (\text{Forward Bias})$$

$$V_{CB} = 1.5 \text{ V} \quad (\text{Reverse Bias})$$

For $V_{CE(\text{min})}$

$$V_{BE} = 0.8 \text{ V} \quad (\text{Forward Bias})$$
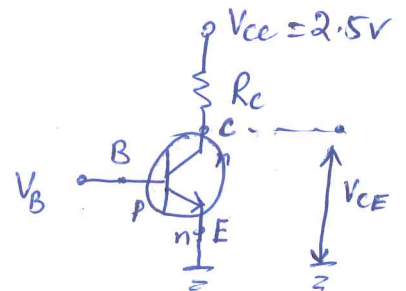
$$V_{CB} = 0.4762 \text{ V} \quad (\text{Reverse Bias})$$



→ The transistor remains in forward active region and behaves as an amplifier.



Habib University

Electrical Engineering Department

Dhanani School of Science & Engineering

Course	EE – 211 – Basic Electronics
Semester	Fall 2022
Section	Section L2
Exam	Quiz – 3b
Instructor	Dr. Ahmad Usman
Total Marks	10

Question – 1 (Points: 1.5 + 5 + 1.5 + 2)


Consider an npn transistor-based amplifier circuit, biased in common emitter configuration, and having the following parameters: $V_{CC} = 2.5 \text{ V}$, $I_S = 3 \times 10^{-16} \text{ A}$, $R_C = 75$, $V_{BE} = 700 \text{ mV}$, $\beta = 150$. The amplifier is having a microphone attached at the input (i.e., base terminal) and the amplified output is observed at the collector terminal.

- Draw the circuit diagram of the amplifier circuit clearly representing each of the important components.
- Calculate I_C , I_B , I_E , V_{CE} , g_m , and r_π .
- Draw the equivalent small-signal model of the transistor. Assume no-early effect.
- Assuming a 2 mV of input signal at the microphone, calculate the amplified signal voltage at the output.

*Bonus: (Points: 3)

Does the input signal qualifies as a small-signal? Calculate the voltage swing at the output with respect to the Q-point of the circuit. Does the transistor remain in forward active region of operation or not? Use your calculations to justify your answer.

(a)

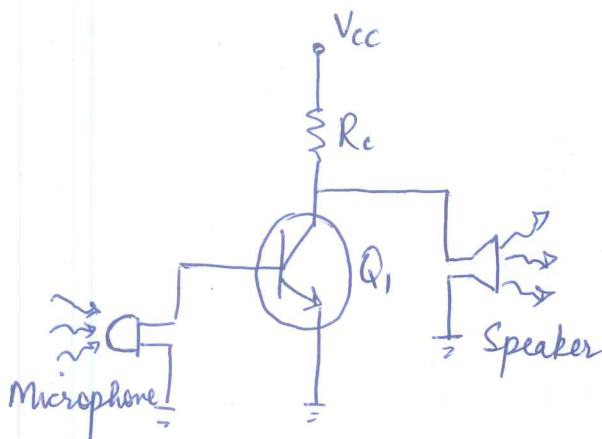

$$I_C = 0.1478 \text{ mA}$$

$$I_B = I_C / \beta = 0.985 \mu\text{A}$$

$$I_E = I_C + I_B = 1.48708 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 2.4889 \text{ V}$$


$$g_m = \frac{I_C}{V_T} = 0.00568 \text{ S}$$

$$r_\pi = \beta / g_m = 26.387 \text{ k}\Omega$$

(b) Assuming $V_T = 26 \text{ mV}$

$$I_C = I_S \exp(V_{BE} / V_T)$$

(c)

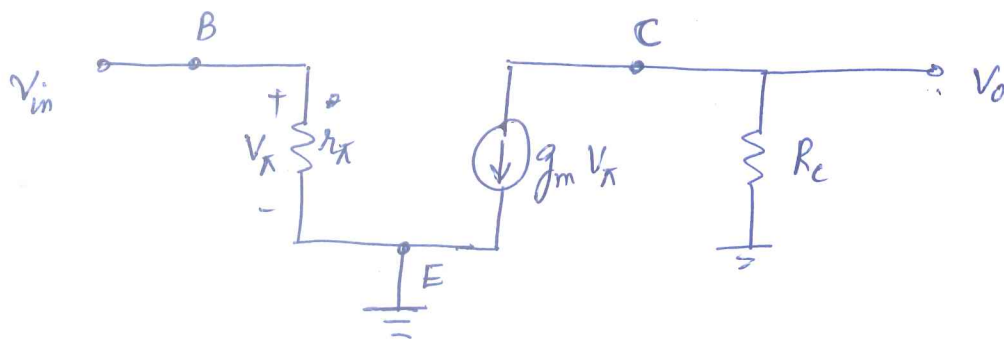

$$\begin{aligned} \Delta i_c &= g_m \Delta V_{BE} \\ &= (0.0568) (2\text{m}) \end{aligned}$$



$$\Delta i_c = \boxed{0.1136 \text{ mA}}$$

$$\begin{aligned} \Delta V_{out} &= (\Delta i_c) R_C \\ &= \boxed{8.52 \text{ mV}} \end{aligned}$$

The voltage is amplified by a factor of 4.26

BONUS

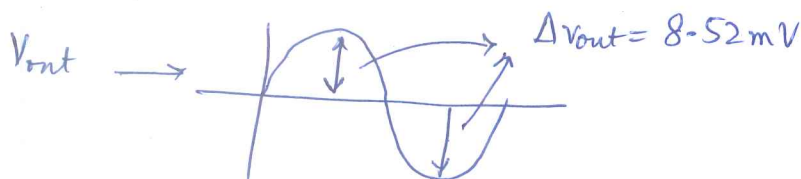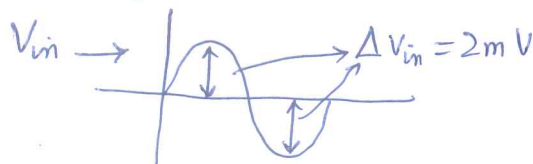- The input is less than 1% of the V_{CC} . It qualifies as a small signal



$$\boxed{V_{CE,Q} = 2.4889 \text{ V}}$$

$$\begin{aligned} V_{CE(\text{max})} &= 2.49742 \text{ V} \\ V_{CE(\text{min})} &= 2.4803 \text{ V} \end{aligned}$$

For $V_{CE(\text{max})}$

$$V_{BE} = 700 \text{ mV} \text{ (Forward Bias)}$$

$$V_{CB} = 1.7974 \text{ (Reverse Bias)}$$

For $V_{CE(\text{min})}$

$$V_{BE} = 700 \text{ mV} \text{ (Forward Bias)}$$

$$V_{CB} = 1.7803 \text{ (Reverse Bias)}$$

→ The transistor remains in forward active region and behaves ~~as~~ as an ~~amplifier~~ amplifier.